

Tyler Thompson

ECE 3570 Lab 3a

10-bit Instruction Set Architecture CPU - Single-Cycle CPU

March 12th, 2018

## Critical Path Delay

**Register File:** 6.8ns

**ALU:** 7.9ns (Longest Case)

**Fetch Unit:** 3.9ns

**Control Unit:** 6.02ns

**CPU Module:** 5.17ns

## Clock Period

Due to the ALU having a the longest critical path delay, the clock period was chosen to be **8ns**. This is the minimum clock period time. The clock cycle time was minimized by having the positive edge of the clock start the clock period. Register are read at the positive edge, so their contents can be sent to the ALU immediately. Since the ALU is the slowest component, feeding it input at the beginning of the clock cycle allows the cycle time to be minimized to the critical path delay of the ALU. This may change once memory is implemented.


## Design Changes



1. The set less than (slt) instruction was changed to compare (cmp). The compare instruction can determine if a number is greater than, less than, or equal to another number.
2. The jump register (jr) instruction was added to help support function call returning.
3. The two's complement (tcp) instruction was added to help deal with negative numbers. It uses the same op code as the addi instruction, but is only called if the immediate value of the instruction is set to negative zero (100).
4. All of the modules in Lab 2 were slightly modified in order to remove latches from their schematics. These changes did not affect the behavior of the modules in the simulator.
5. An input signal was added to the fetch unit that is fed by the result of the ALU. This allows the fetch unit to know when branch instructions execute successful and is more efficient than adding more control lines to the control unit.



## 10-Bit ISA Reference Sheet



Instructions						
Name	Description	Format	RTL	Syntax	OP Code (hex)	Function Code (hex)
add	Add two values in registers together	R	if MEM[PC] == ADD rs rt rd [rs] <= [rt] + [rd] PC <= PC + 1	add \$rs, \$rt, \$rd	0x0	
addi	Add a 3-bit signed constant to a value in a register	I	if MEM[PC] == ADDI rs rt imm [rs] <= [rt] + sign-ext(imm) PC <= PC + 1	addi \$rs, \$rt, imm	0x4	
tcp	Take the two's complement of a value in a register Imm value should be set to 100 (-0) to differentiate from addi	I	if MEM[PC] == TCP rs rt [rs] <= ~[rt] + 1 PC <= PC + 1	tcp \$rs, \$rt	0x4	
sw	Store a word in memory	I	if MEM[PC] == SW rt offset(base) address = sign-extend(offset) + [base] MEM[address] <= [rt] PC <= PC + 1	sw \$rs, M(\$rt)	0x5	
lw	Load a word from memory	I	if MEM[PC] == LW rt offset(base) address = sign-extend(offset) + [base] [rt] <= MEM[address] PC <= PC + 1	lw \$rs, M(\$rt)	0x6	
sll	Shift left logical	R	if MEM[PC] == SLL rd rs rt [rd] <= [rs] << [rt] PC = PC + 1	sll \$rd, \$rs, \$rt	0x1	
cmp	Compare	R	if MEM[PC] == CMP rd rs rt [rd] <= [rs] < [rt] - 1 [rd] <= [rs] == [rt] - 0 [rd] <= [rs] > [rt] - 2 PC = PC + 1	cmp \$rd, \$rs, \$rt	0x2	
beq	Branch equal	R	if MEM[PC] == BEQ rd rs rt if [rs] == [rt] PC <= PC + 4 + [rd]	beq \$rd, \$rs, \$rt	0x3	
jal	Jump and link	J	if MEM[PC] == JAL address [ra] <= PC + 1 PC <= PC + address	jal Label	0x7	0x2
j	Jump	J	if MEM[PC] == J address PC <= PC + address	j Label	0x7	0x1
jr	Jump Register	J	if MEM[PC] == JR \$reg PC <= \$reg	jr \$reg	0x7	0x0
halt	Halt the machine	J	if MEM[PC] == HALT PC <= 0x0	halt	0x7	0x3

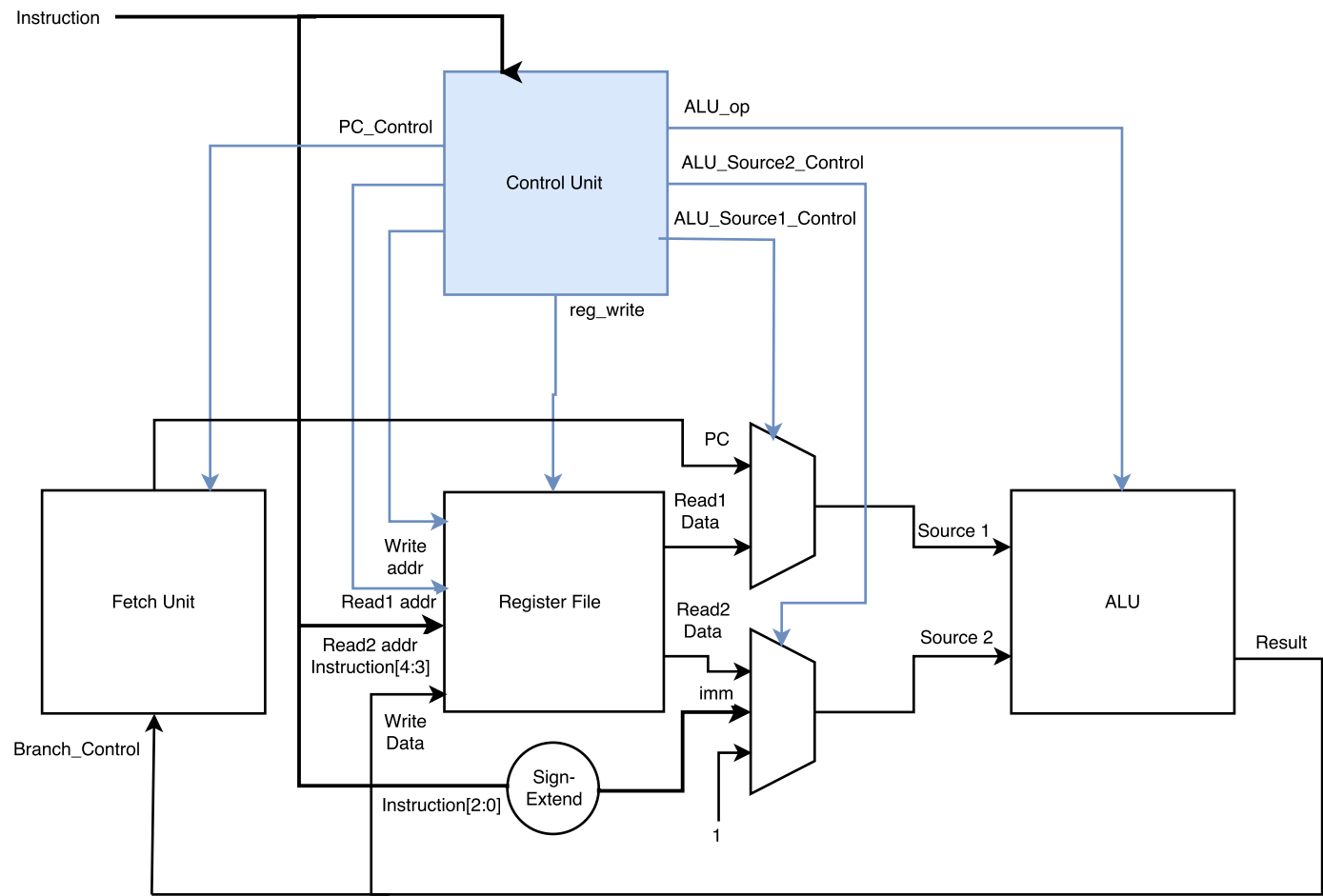10-Bit Instruction Set Architecture  
Datapath Schematic




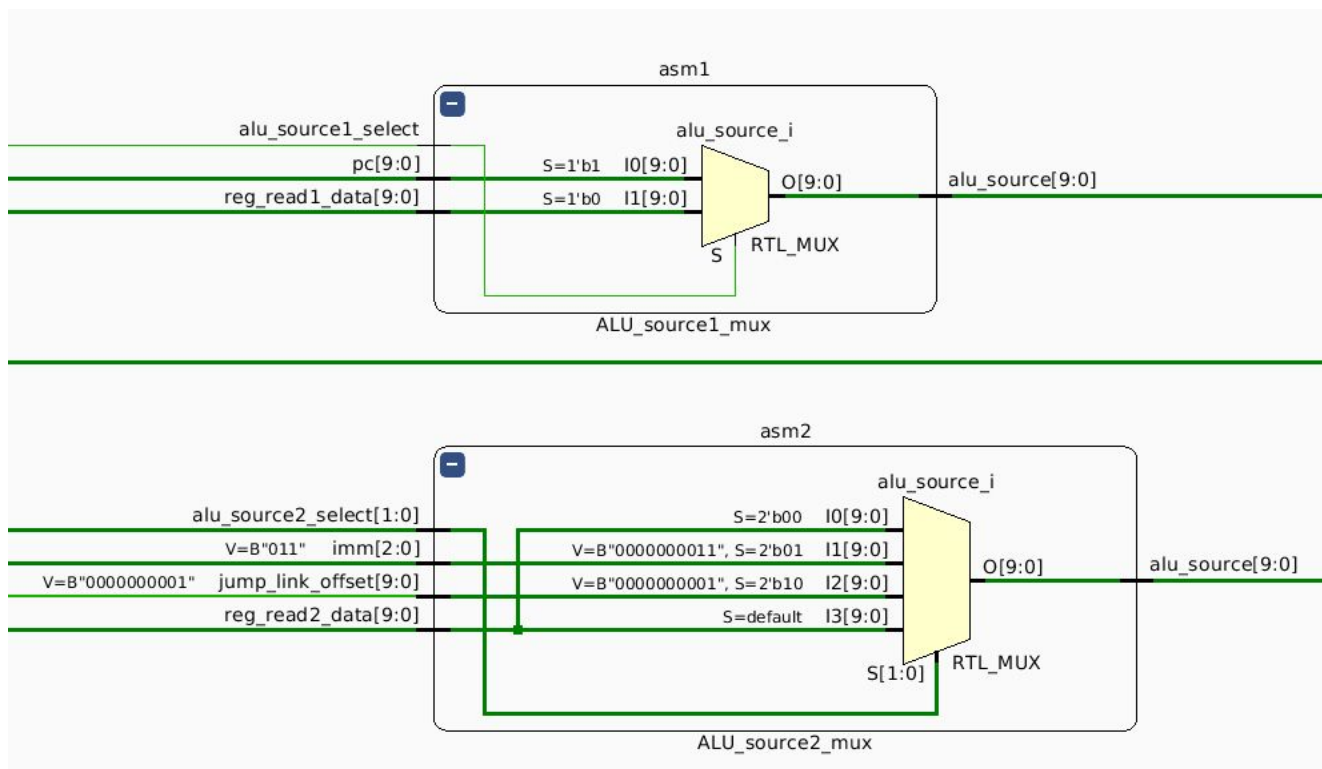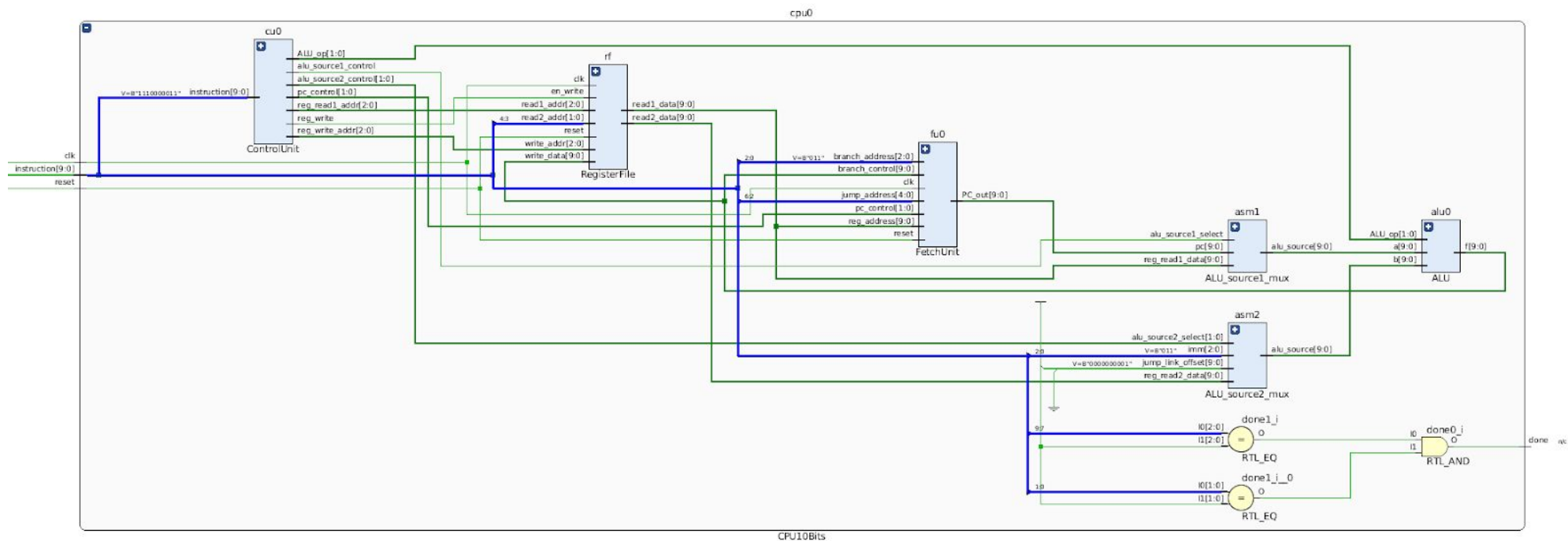

 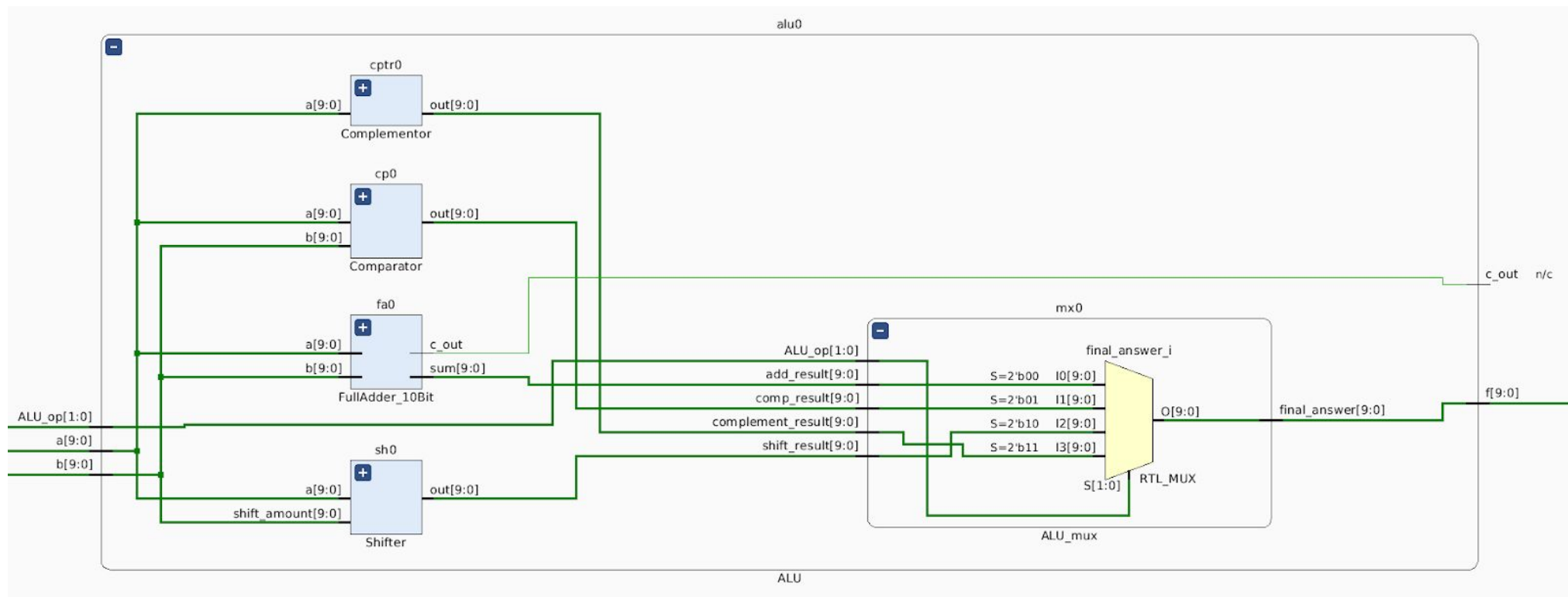


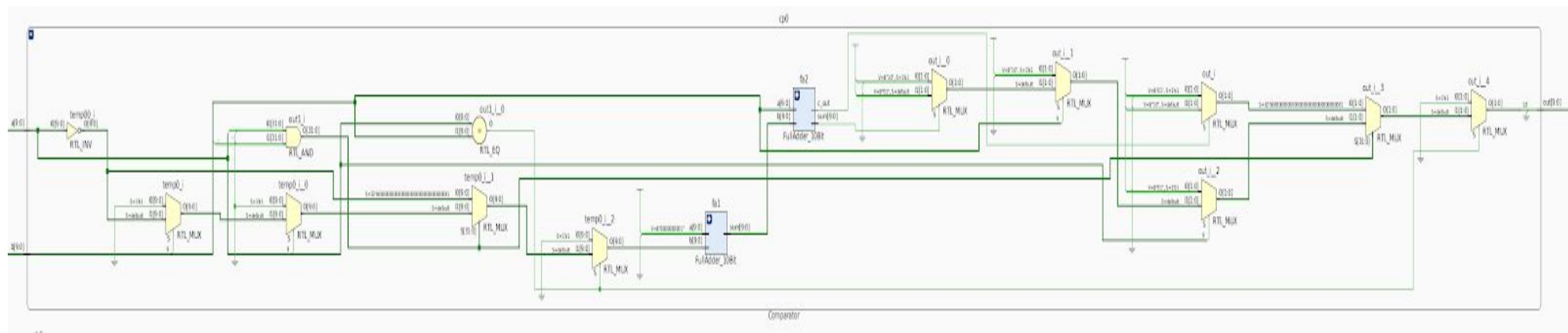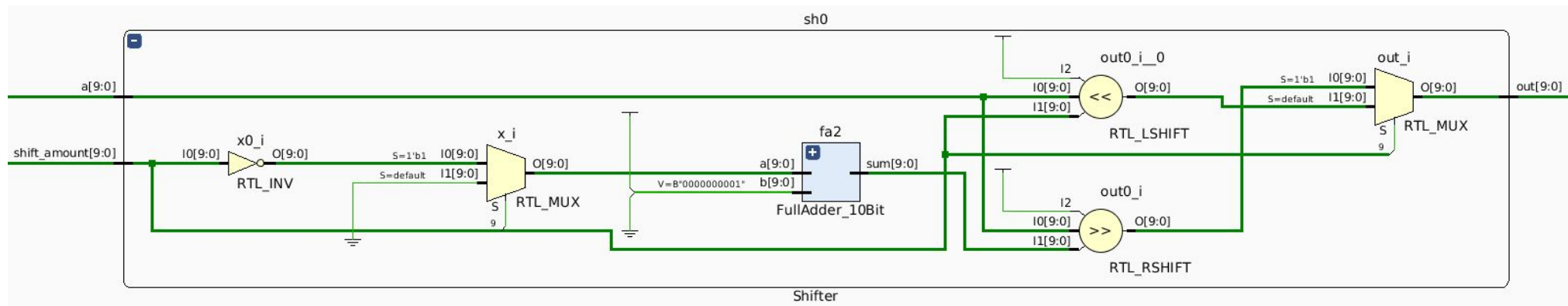

Comparator

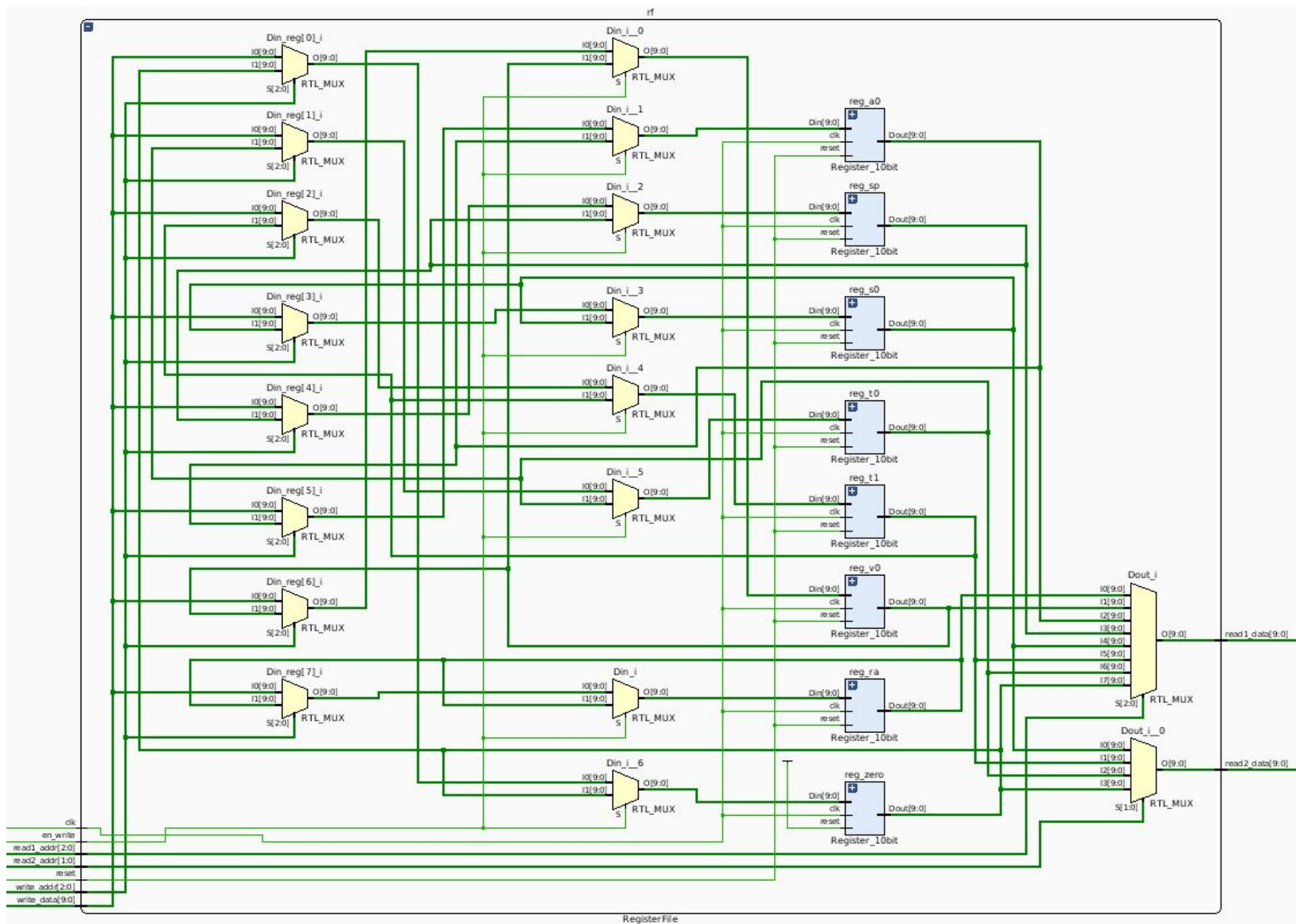



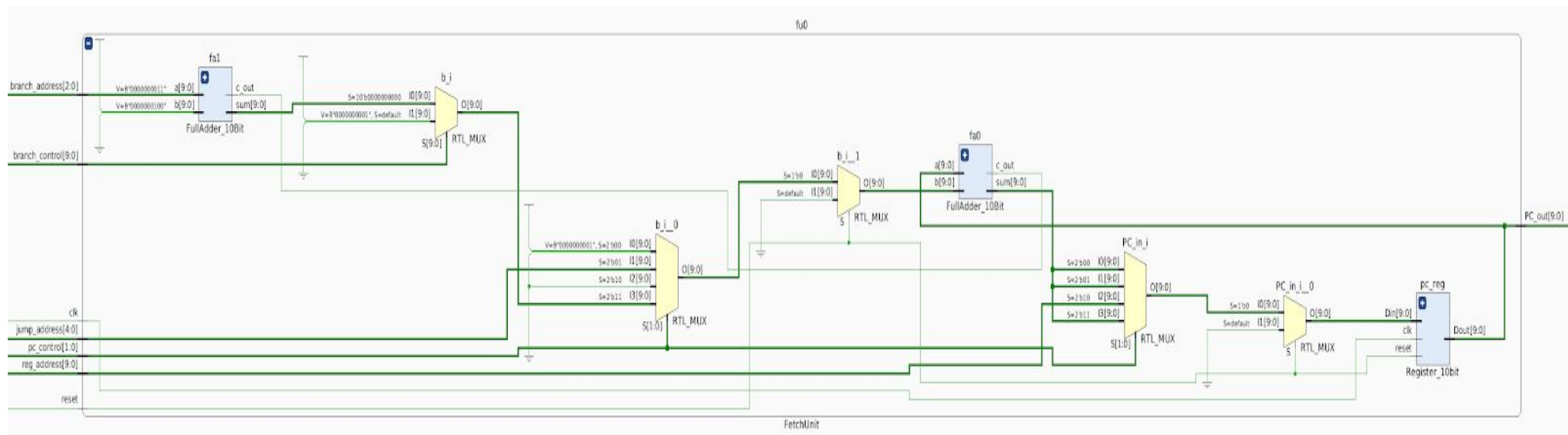


Fetch Unit


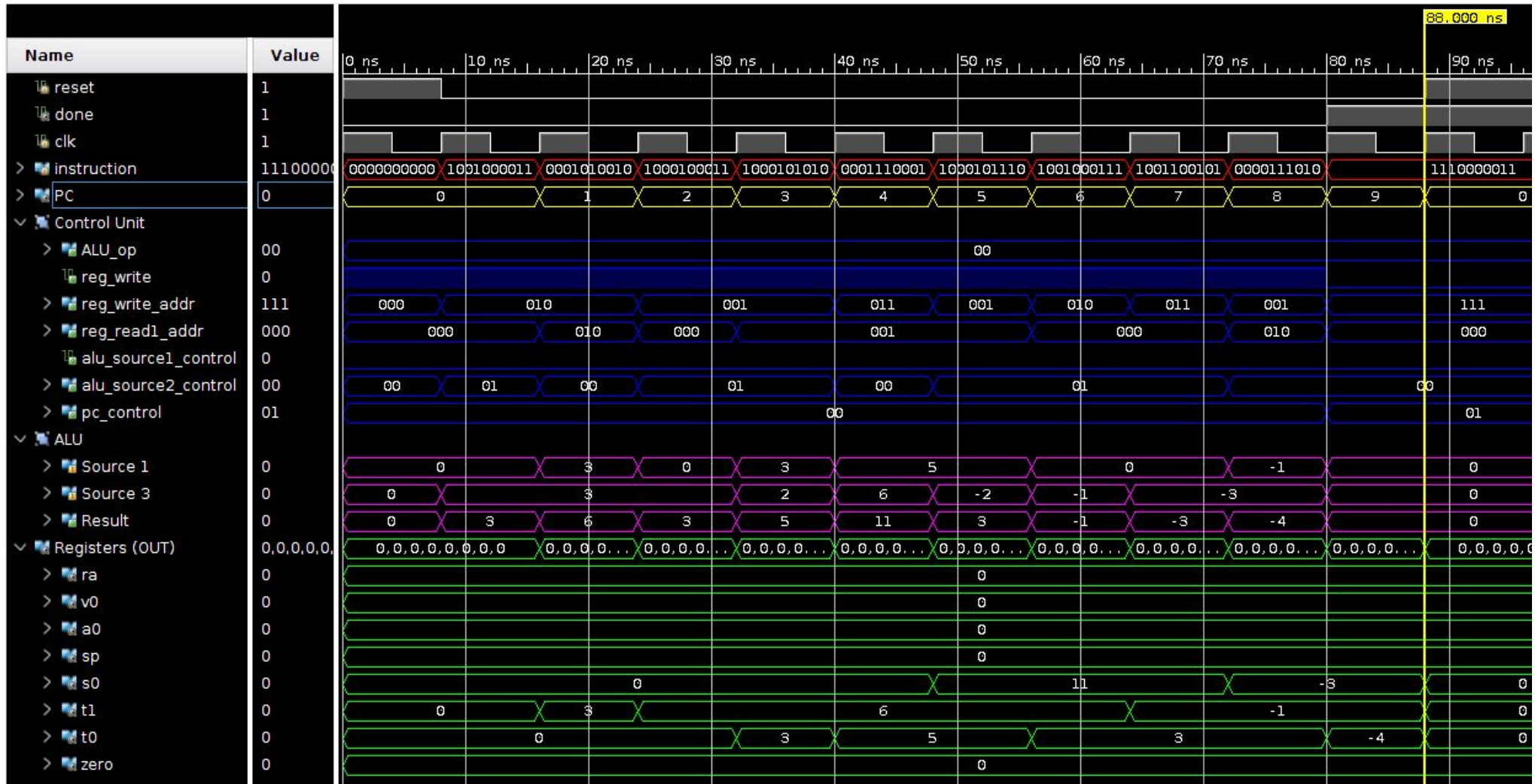
## ADD and ADDI Instruction Test


☐ Clock/Reset/Done   
 ☒ Instruction   
 ☒ Program Counter   
 ☒ Control Signals   
 ☒ ALU Signals   
 ☒ Register Contents


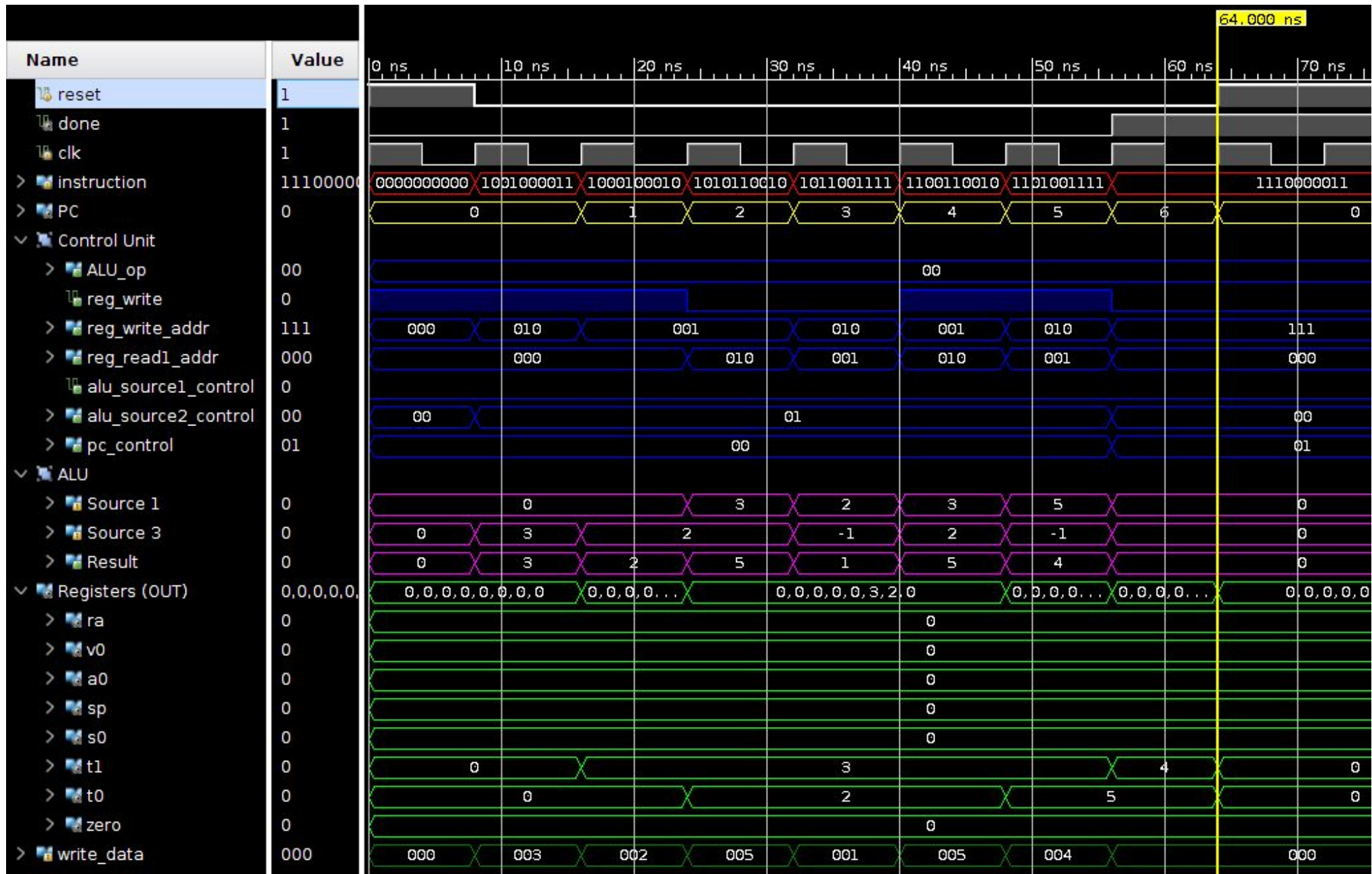
## LW and SW Instruction Test

(Because there is no memory, lw stores the memory address in the destination register and sw attempts to do the same, but fails to write to the register because the reg\_write signal disables writing.)

☐ Clock/Reset/Done  
 ☒ Instruction  
 ☒ Program Counter  
 ☒ Control Signals  
 ☒ ALU Signals  
 ☒ Register Contents





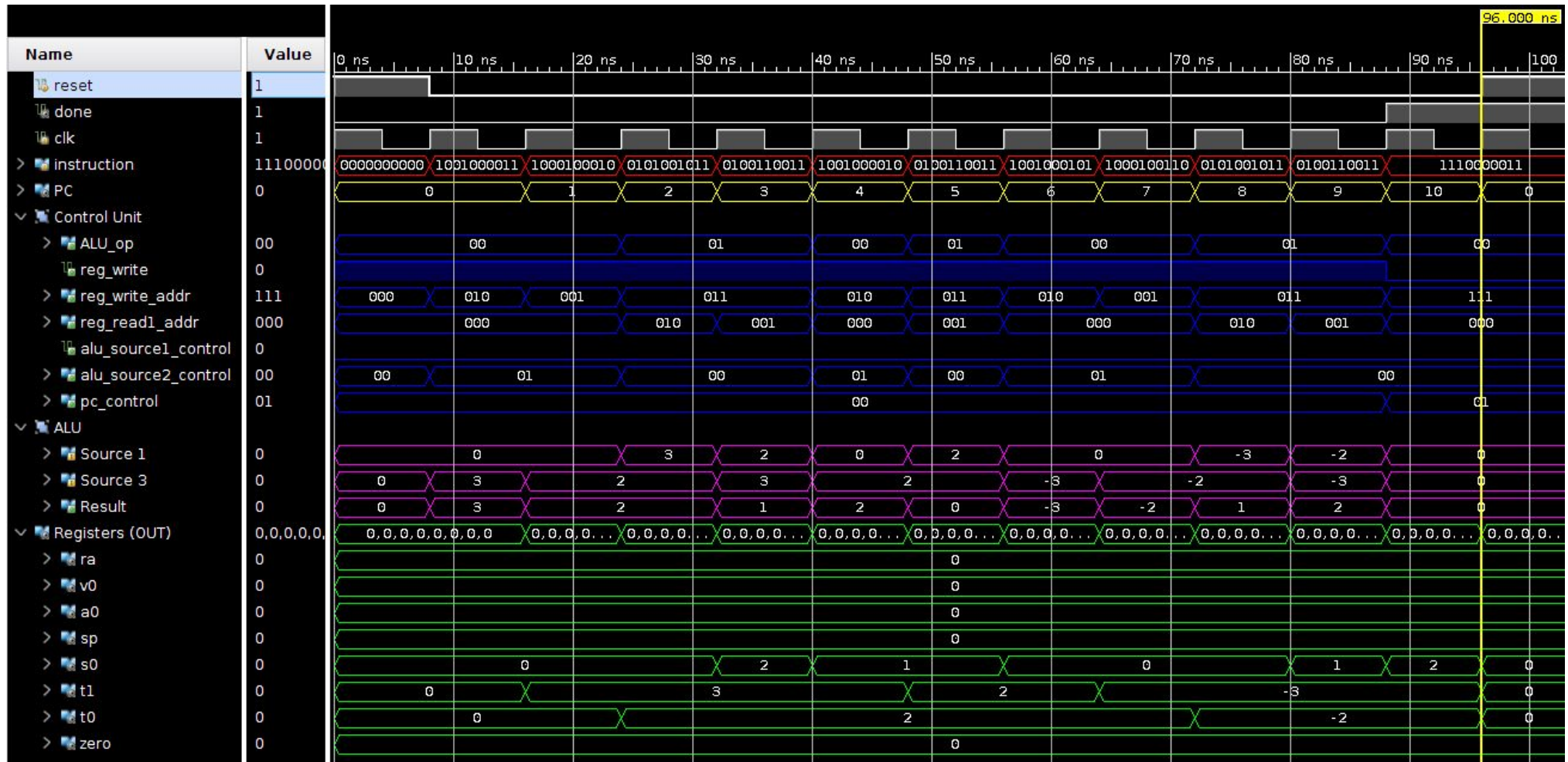
## CMP (Compare) Instruction Test


ALU Compare Result: (1):  $a < b$    (0):  $a == b$    (2):  $a > b$

□ Clock/Reset/Done    ■ Instruction    ■ Program Counter    ■ Control Signals    ■ ALU Signals    ■ Register Contents



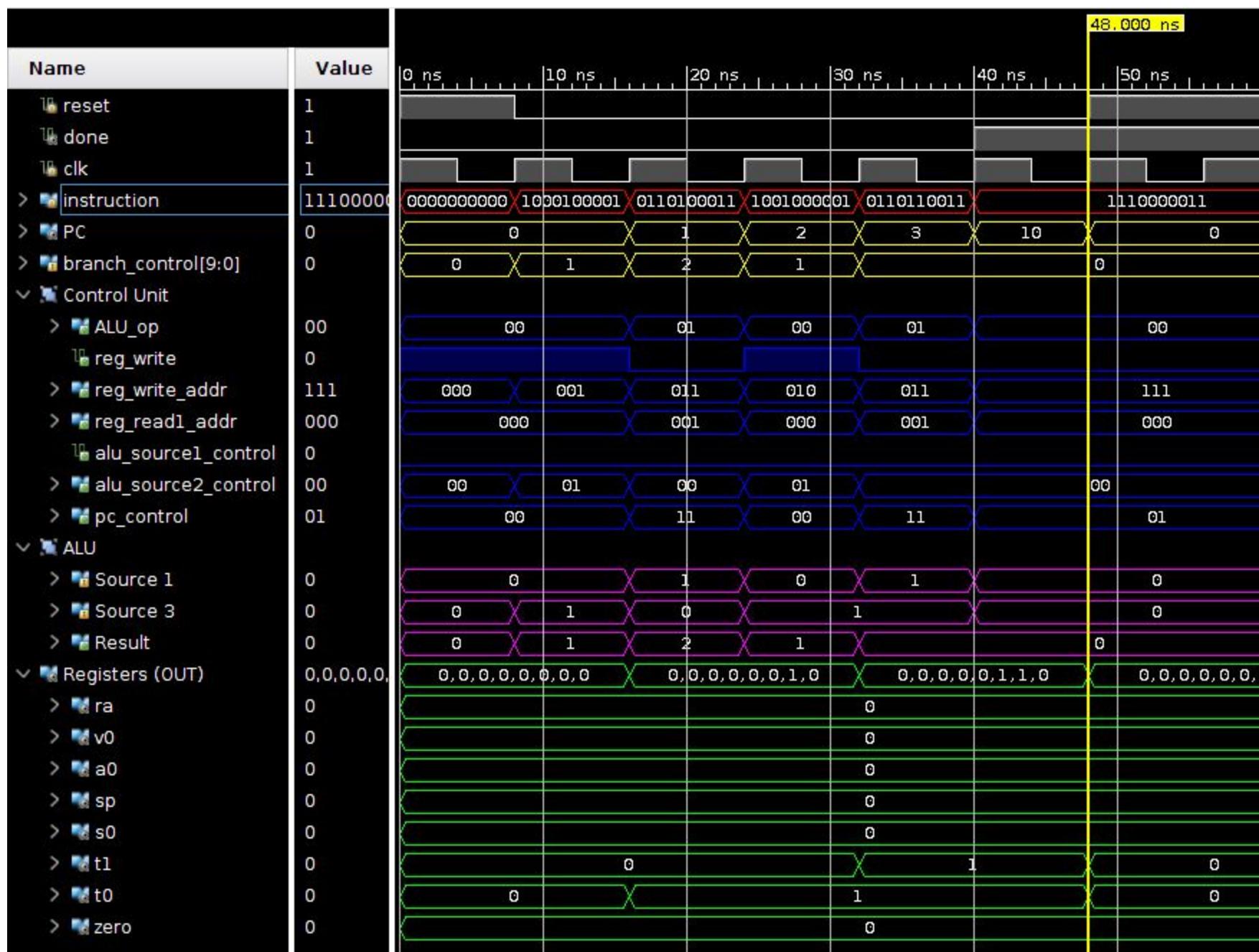
## BEQ Instruction Test

□ Clock/Reset/Done    ■ Instruction    ■ Program Counter    ■ Control Signals    ■ ALU Signals    ■ Register Contents


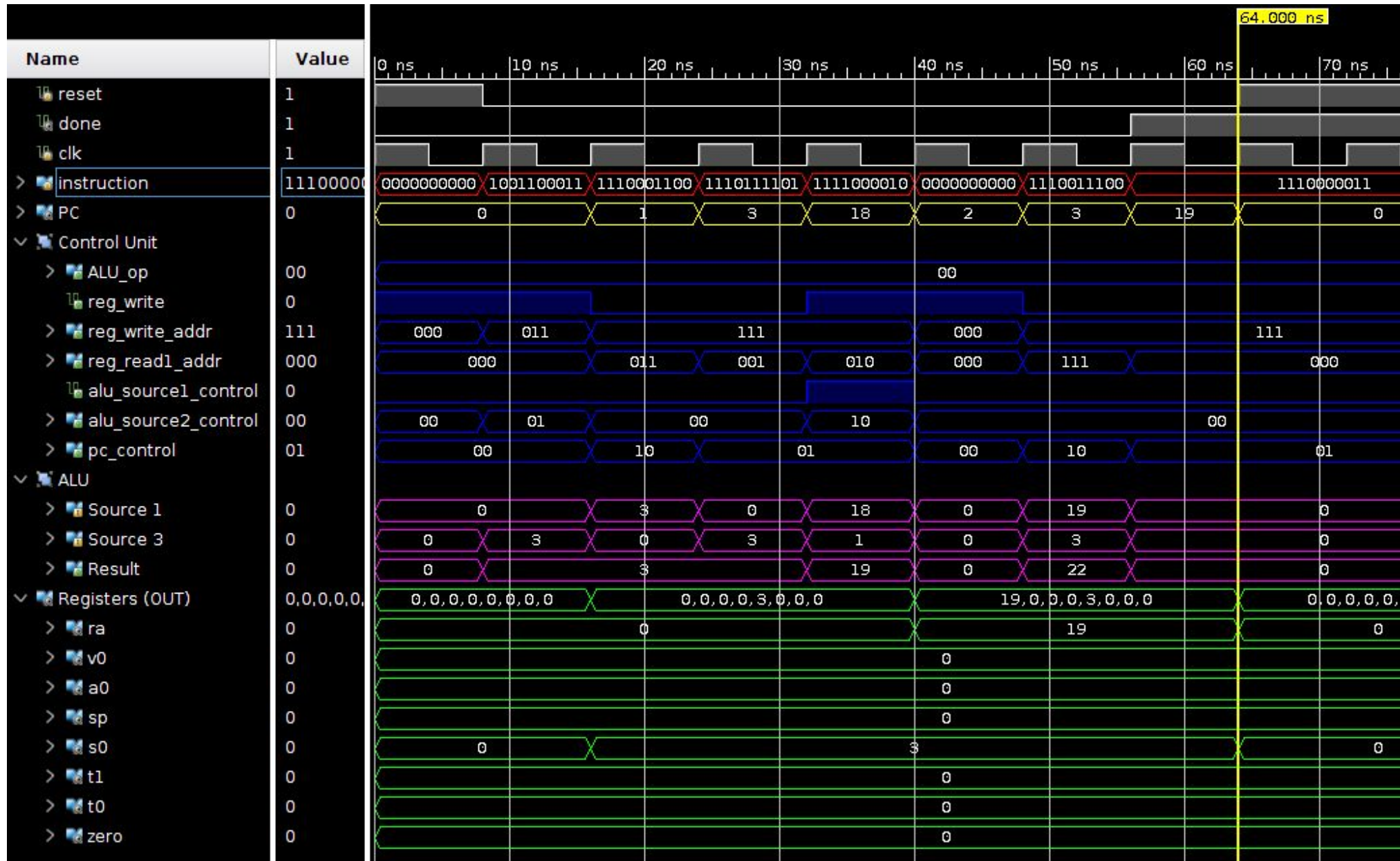
## J, JR, and JAL Instruction Test


☐ Clock/Reset/Done  
 ☒ Instruction  
 ☒ Program Counter  
 ☒ Control Signals  
 ☒ ALU Signals  
 ☒ Register Contents




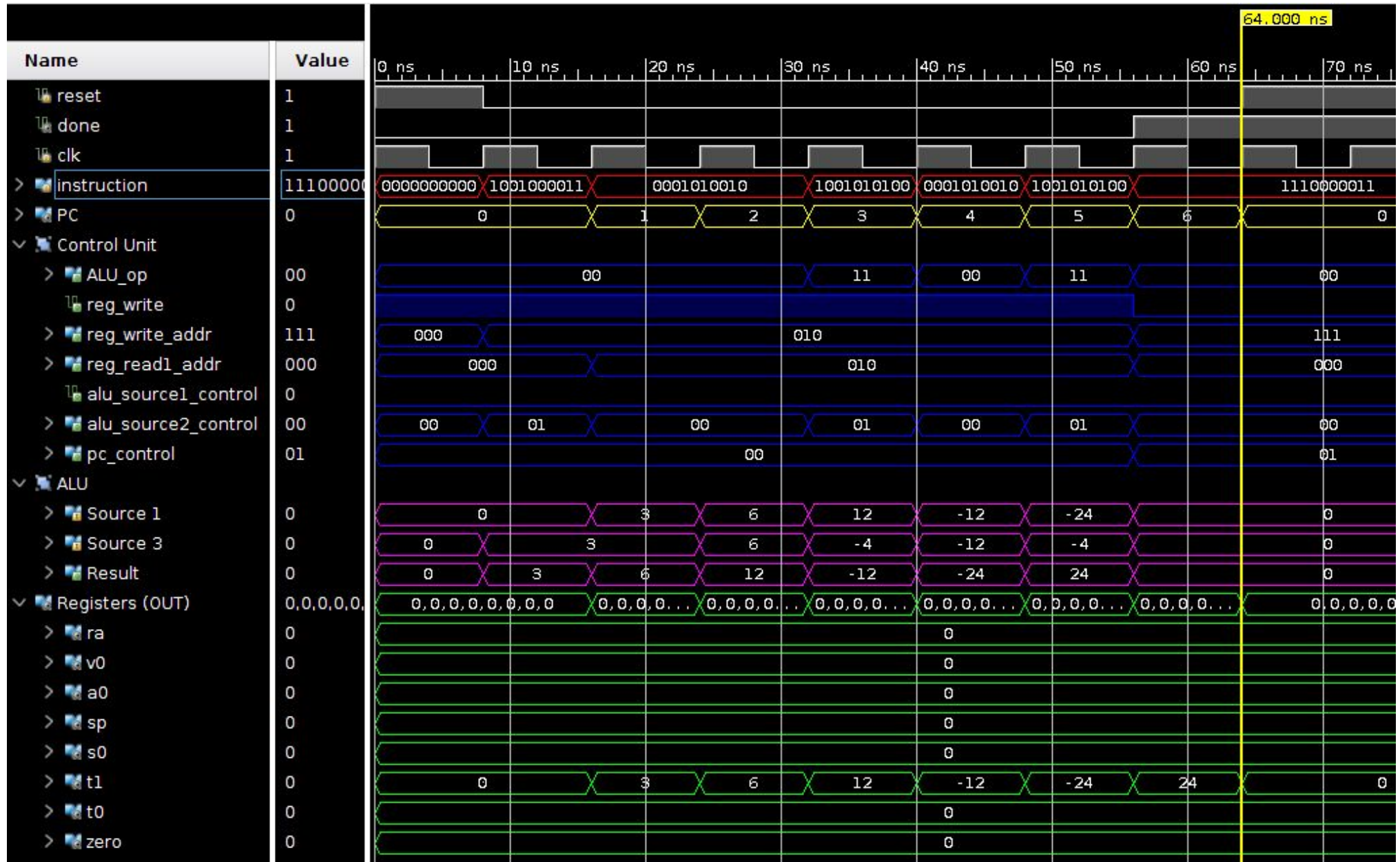
## TCP (Two's Complement) Instruction Test


☐ Clock/Reset/Done  
 ☒ Instruction  
 ☒ Program Counter  
 ☒ Control Signals  
 ☒ ALU Signals  
 ☒ Register Contents





 
## Control Unit Module Test (1 of 2)

■ Instruction ■ Instruction Decode ■ Control Signals


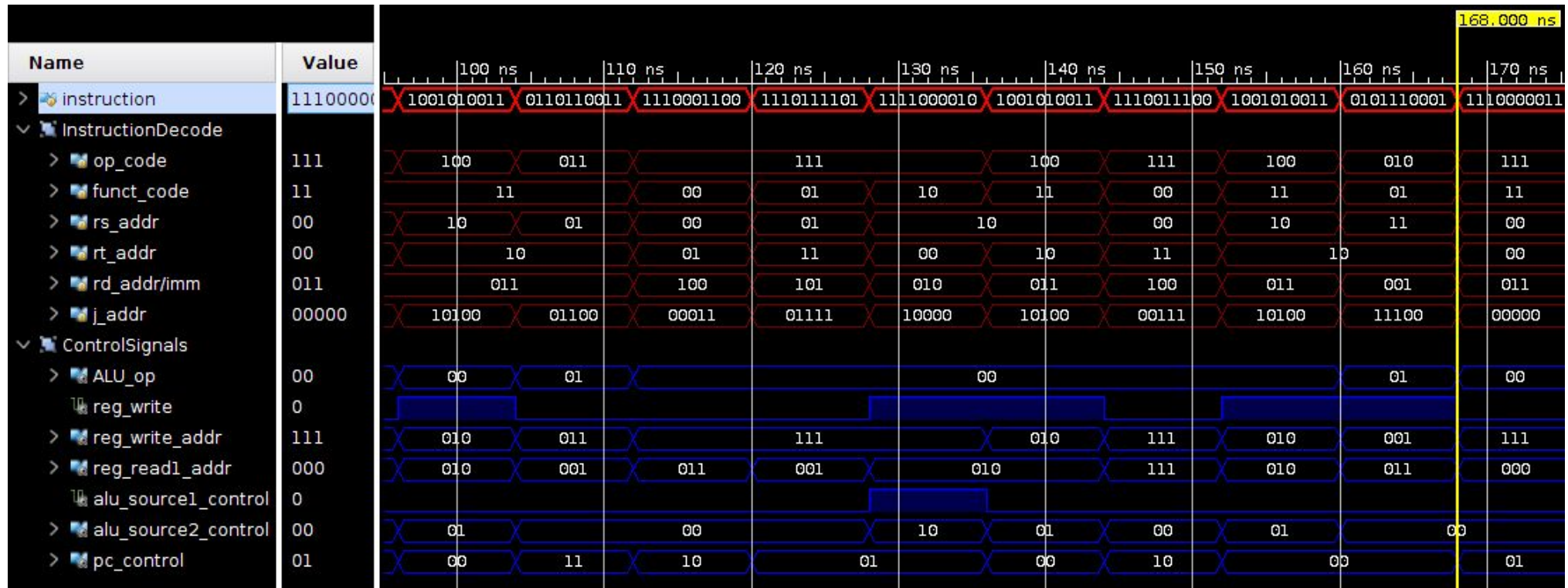
## Control Unit Module Test (2 of 2)

■ Instruction   
 ■ Instruction Decode   
 ■ Control Signals



```

; Tyler Thompson
; ECE3570 Lab3a
; 2/6/2018
; Program 3 re-written for memoryless execution
; This program was modified for each test to accommodate
; different values of x and y

1001000011      addi $t1, $zero, 3      ;$t1=x=3
0011000101      sll $a0, $t1, $zero    ;store original x in $a0
1001100010      addi $s0, $zero, 2
1001111010      addi $s0, $s0, 2      ;$s0=y=4
0000111000      add $t0, $s0, $zero    ;$t0=4

0111000000      beq $t1, $zero, 0      ;if x==0, pc=pc+4
0001111001      add $s0, $s0, $t0      ;y=y+4
1001010111      addi $t1, $t1, -1      ;x--
1111110101      j -3                  ;pc=pc-3

0001000101      add $t1, $zero, $a0    ;load original x
0101000010      cmp $t1, $t1, $zero
1000100001      addi $t0, $zero, 1
0110110101      beq $t0, $t1, -2      ;if x is pos, pc=pc+2
1001111100      tcp $s0, $s0          ;two comp of y
1001111110      addi $s0, $s0, -2
1001111110      addi $s0, $s0, -2      ;y=y-4
0011100110      sll $v0, $s0, $zero    ;f=(x*y)-4


1110000011      halt

```
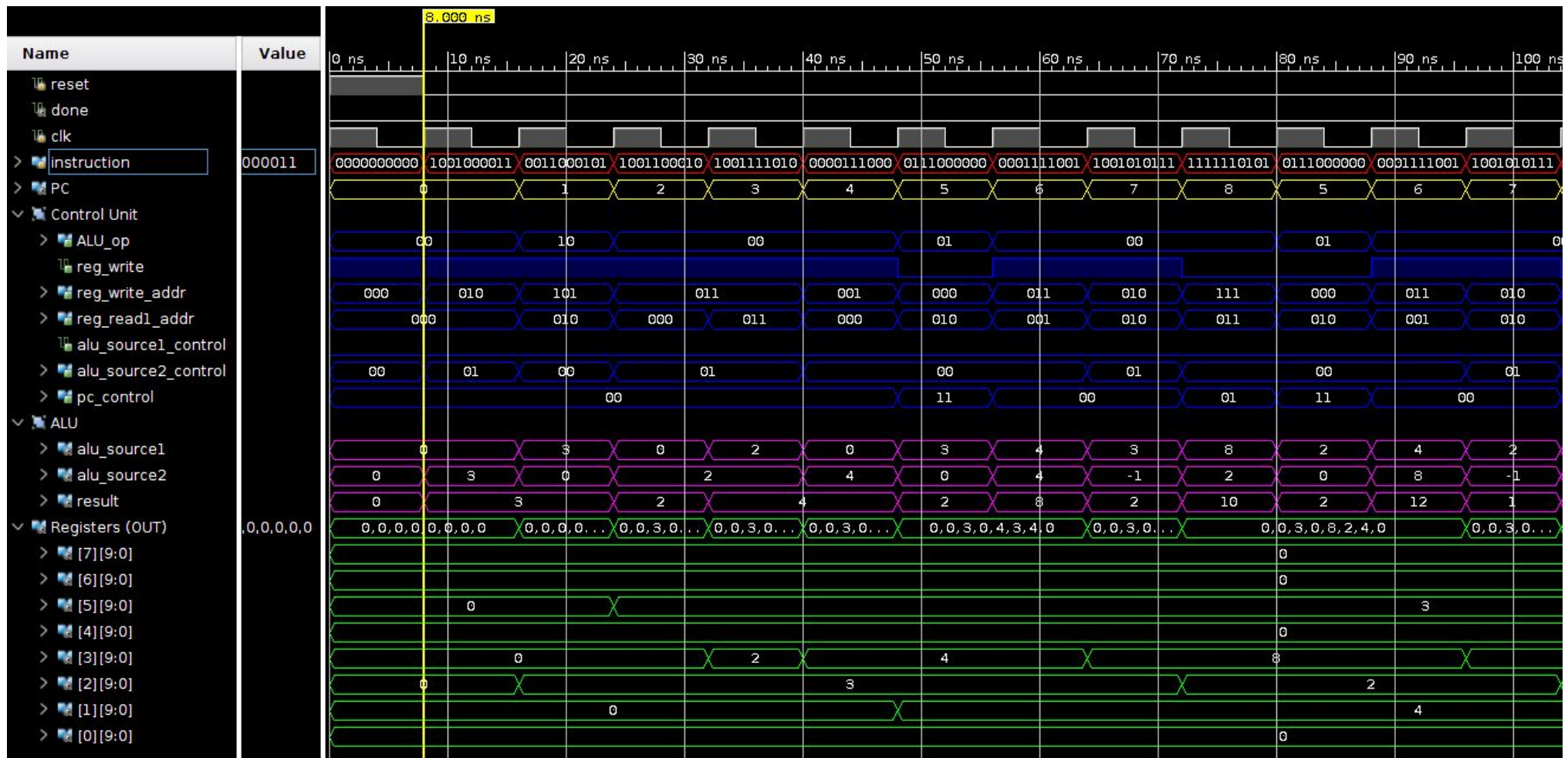
# Program 3 Test Run 1 (1 of 2)

X = 3 Y = 4 F = 8

F is stored into v0 at the end of the program



### Program 3 Test Run 1 (2 of 2)

The timing diagram illustrates the execution of the first instruction (000011) in a 5-stage MIPS processor. The time axis ranges from 110 ns to 180 ns. A yellow vertical line marks 176.000 ns.

**Instruction:** 000011 (R-type)

**PC:** 7

**Control Unit:**

- ALU\_op: 00, 01, 00, 01, 00, 10
- reg\_write: 111, 010, 001, 101, 011, 110
- reg\_write\_addr: 011, 101, 010, 000, 001, 011
- reg\_read1\_addr: 01, 00, 11, 00
- alu\_source1\_control: 00, 01, 00, 01
- alu\_source2\_control: 01, 00, 11, 00
- pc\_control: 01, 00, 11, 00

**ALU:**


- alu\_source1: 12, 3, 0, 1, 12, 10, 8
- alu\_source2: 1, 0, 1, 2, -2
- result: 13, 3, 2, 1, 10, 8

**Registers (OUT):** 0,0,0,0,0


- [7][9:0]: 0
- [6][9:0]: 8
- [5][9:0]: 3
- [4][9:0]: 0
- [3][9:0]: 12, 10, 8
- [2][9:0]: 2, 1, 3, 2
- [1][9:0]: 4, 1
- [0][9:0]: 0



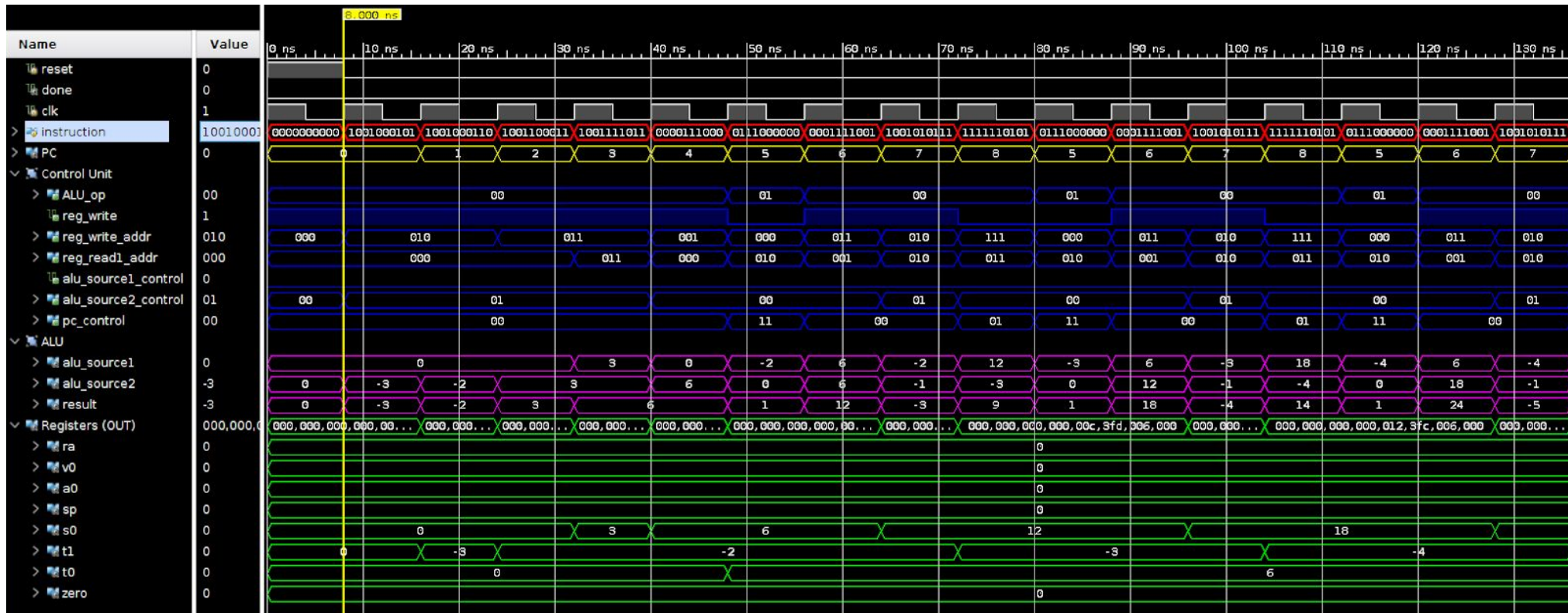X = -5 Y = 6 F = -34  
F is stored into v0 at the end of the program




## Program 3 Test Run 2 (2 of 2)

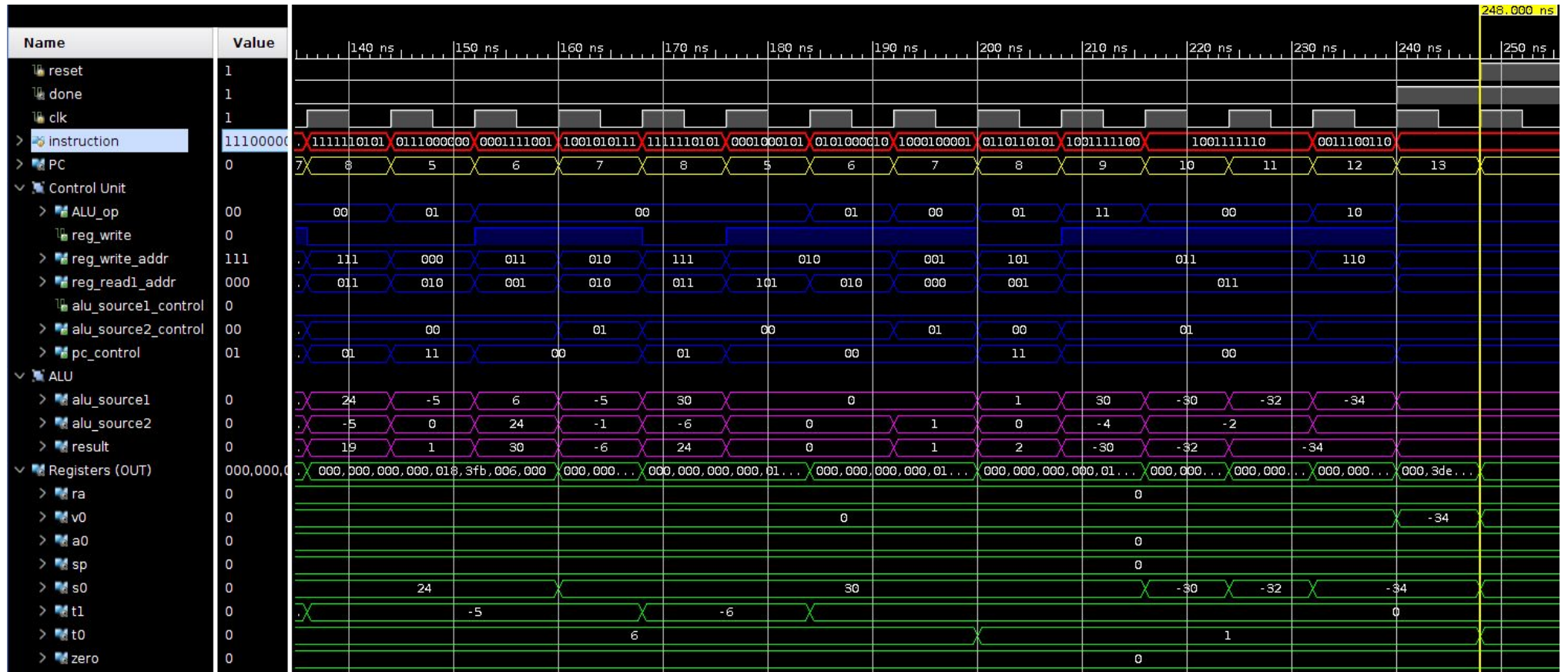
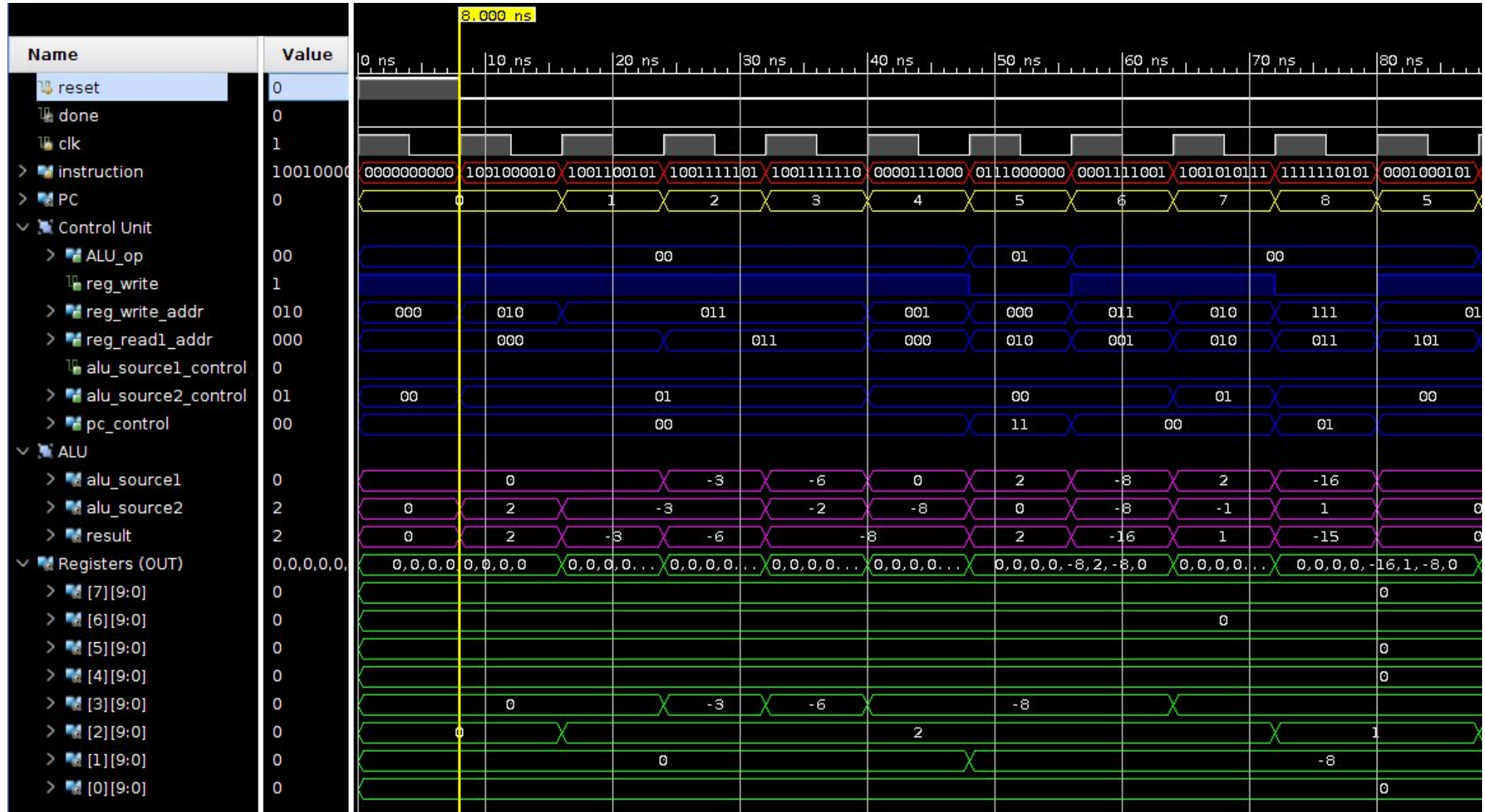
### Program 3 Test Run 3 (1 of 2)


$$X = 2 \quad Y = -8 \quad F = -20$$

F is stored into v0 at the end of the program






# Program 3 Test Run 3 (2 of 2)

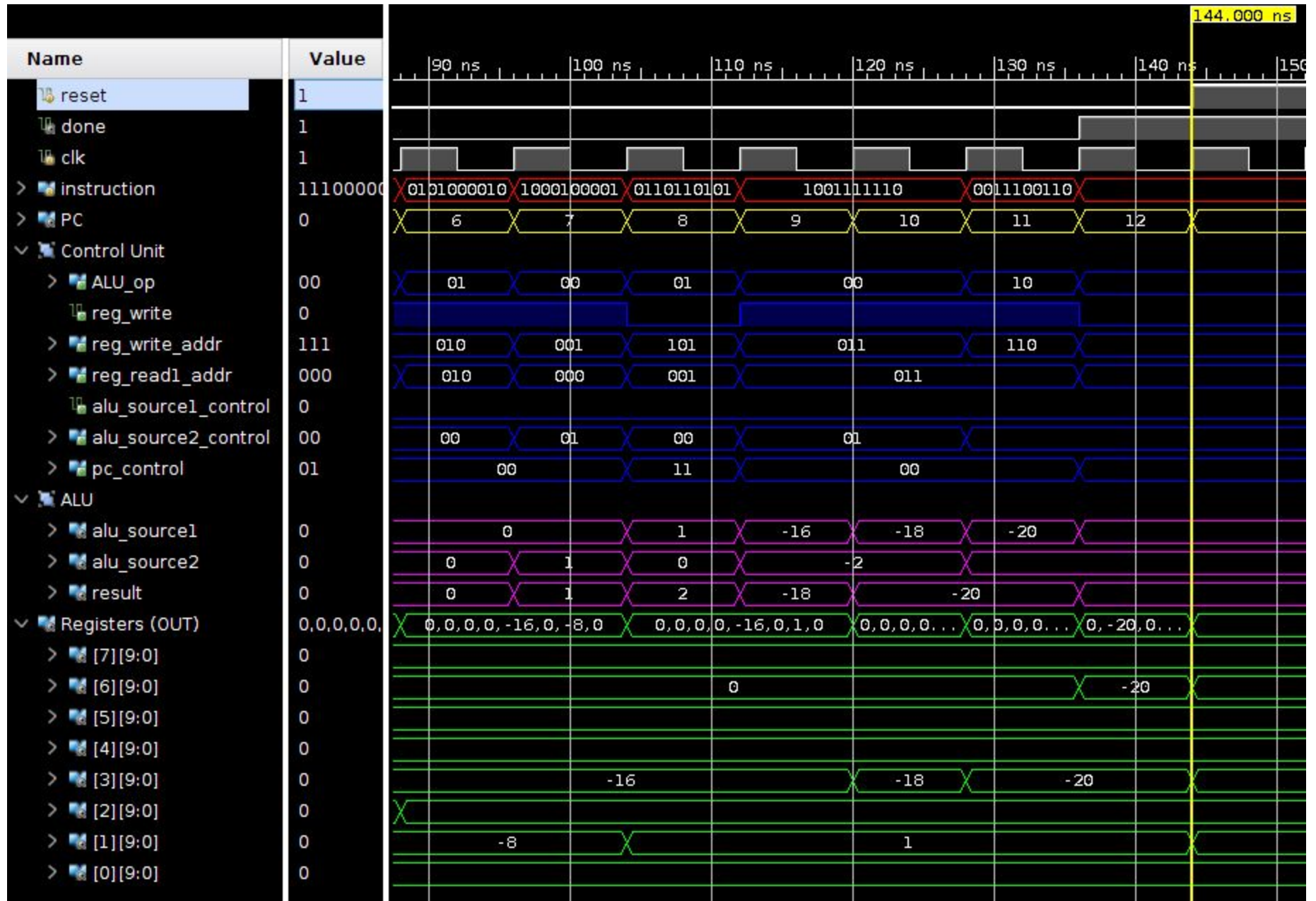

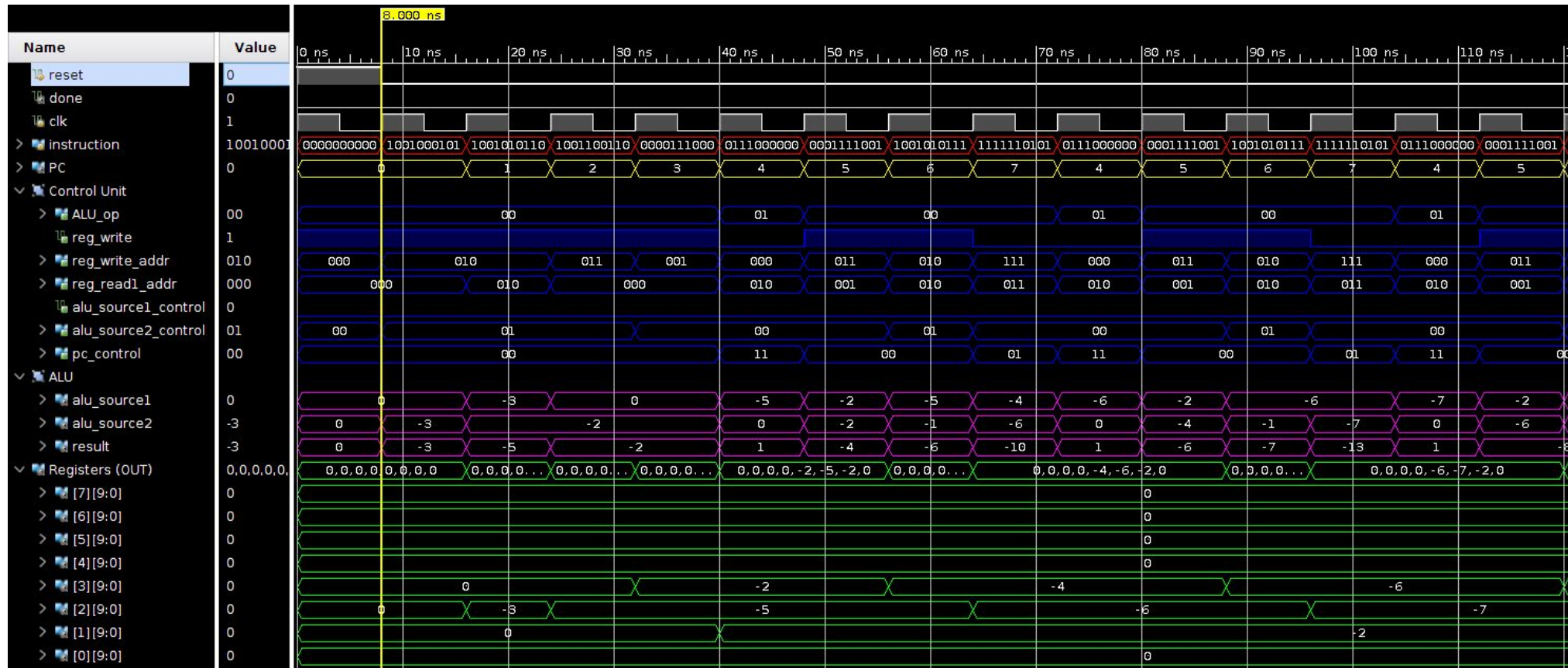
### Program 3 Test Run 4 (1 of 2)

$$X = -5 \quad Y = -2 \quad F = 6$$

F is stored into v0 at the end of the program



# Program 3 Test Run 4 (2 of 2)

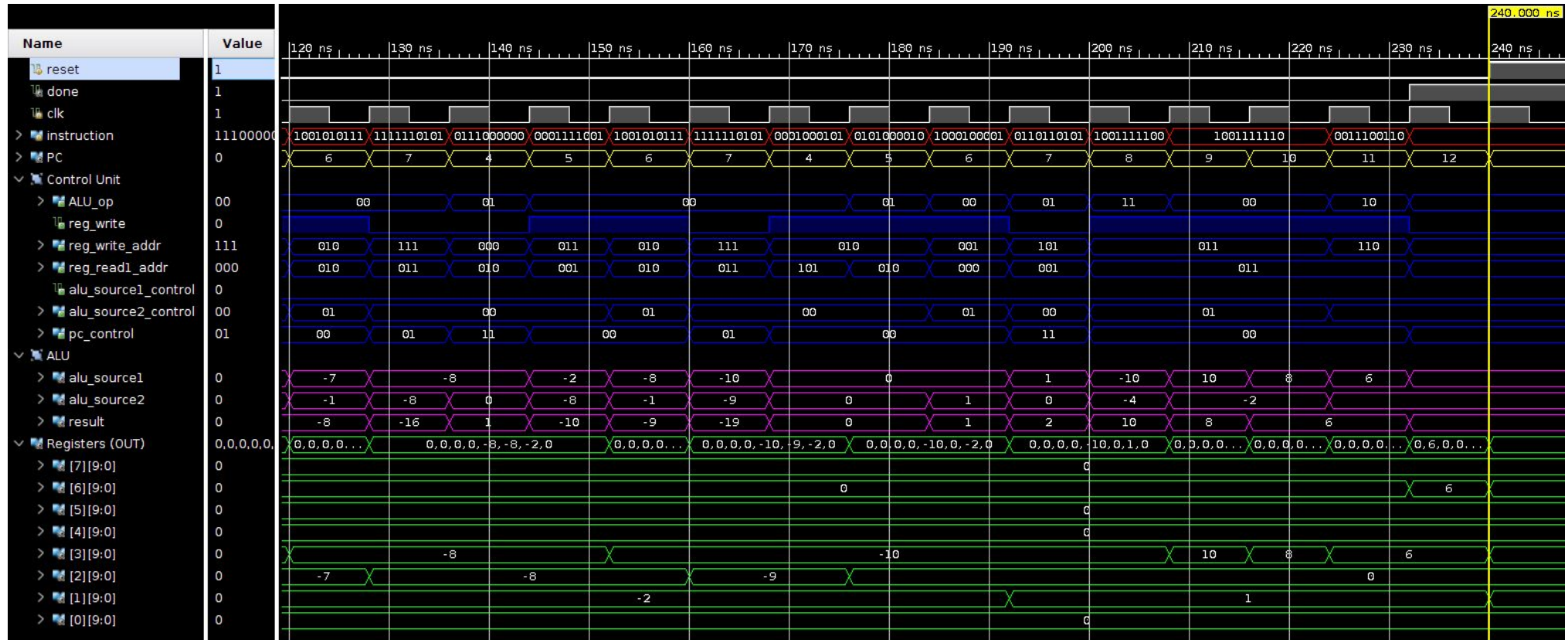

```

`timescale 1ns / 1ns
`include "ALU.v"
`include "Registers.v"
`include "ControlUnit.v"
`include "FetchUnit.v"
/////////////////////////////////////////////////////////////////
// Company: Western Michigan University
// Engineer: Tyler Thompson
//
// Create Date: 02/22/2018 04:42:19 PM
// Design Name:
// Module Name: CPU
// Project Name: ECE 3570 Lab 3a
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module CPU10Bits_jump_test();
    reg clk;
    reg reset;
    reg [9:0] instruction;
    wire done;

    CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

    //toggle clock every 4ns
    always #4 clk = ~clk;

    initial begin
        clk = 1;
        reset = 1;
        instruction = 10'b0000000000; // NOP
        #8;
        reset = 0;

        instruction = 10'b1001100011; // addi $s0, $zero, 3
        #8;
        instruction = 10'b1110001100; // jr $s0
        #8;
        instruction = 10'b1110111101; // j 01111 (15)
        #8;
        instruction = 10'b1111000010; // jal 10000 (-16)
        #8;
        instruction = 10'b0000000000; // NOP
        #8;
        instruction = 10'b1110011100; // jr $ra
        #8;
        instruction = 10'b1110000011; // halt
        #8;
        reset = 1;
    end
endmodule

module CPU10Bits_branch_test();
    reg clk;

```

```

reg reset;
reg [9:0] instruction;
wire done;

CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

//toggle clock every 4ns
always #4 clk = ~clk;

initial begin
    clk = 1;
    reset = 1;
    instruction = 10'b0000000000; // NOP
    #8;
    reset = 0;

    instruction = 10'b1000100001; // addi $t0, $zero, 1
    #8;
    instruction = 10'b0110100011; // beq $t0, $zero, PC=PC+4+3
    #8;
    instruction = 10'b1001000001; // addi $t1, $zero, 1
    #8;
    instruction = 10'b0110110011; // beq $t0, $t1, PC=PC+4+3
    #8;
    instruction = 10'b1110000011; // halt
    #8;
    reset = 1;
end
endmodule

module CPU10Bits_twos_complement_test();
    reg clk;
    reg reset;
    reg [9:0] instruction;
    wire done;

    CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

//toggle clock every 4ns
always #4 clk = ~clk;

initial begin
    clk = 1;
    reset = 1;
    instruction = 10'b0000000000; // NOP
    #8;
    reset = 0;

    instruction = 10'b1001000011; // addi $t1, $zero, 3
    #8;
    instruction = 10'b0001010010; // add $t1, $t1, $t1
    #8;
    instruction = 10'b0001010010; // add $t1, $t1, $t1
    #8;
    instruction = 10'b1001010100; // tcp $t1, $t1
    #8;
    instruction = 10'b0001010010; // add $t1, $t1, $t1
    #8;
    instruction = 10'b1001010100; // tcp $t1, $t1
    #8;
    instruction = 10'b1110000011; // halt
    #8;

```

```

        reset = 1;
    end
endmodule

module CPU10Bits_compare_test();
    reg clk;
    reg reset;
    reg [9:0] instruction;
    wire done;

    CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

    //toggle clock every 4ns
    always #4 clk = ~clk;

    initial begin
        clk = 1;
        reset = 1;
        instruction = 10'b0000000000; // NOP
        #8;
        reset = 0;

        instruction = 10'b1001000011; // addi $t1, $zero, 3
        #8;
        instruction = 10'b1000100010; // addi $t0, $zero, 2
        #8;
        instruction = 10'b0101001011; // cmp $s0, $t1, $t0
        #8;
        instruction = 10'b0100110011; // cmp $s0, $t0, $t1
        #8;
        instruction = 10'b1001000010; // addi $t1, $zero, 2
        #8;
        instruction = 10'b0100110011; // cmp $s0, $t0, $t1
        #8;
        instruction = 10'b1001000101; // addi $t1, $zero, -3
        #8;
        instruction = 10'b1000100110; // addi $t0, $zero, -2
        #8;
        instruction = 10'b0101001011; // cmp $s0, $t1, $t0
        #8;
        instruction = 10'b0100110011; // cmp $s0, $t0, $t1
        #8;
        instruction = 10'b1110000011; // halt
        #8;
        reset = 1;
    end
endmodule

module CPU10Bits_store_load_test();
    reg clk;
    reg reset;
    reg [9:0] instruction;
    wire done;

    CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

    //toggle clock every 4ns
    always #4 clk = ~clk;

    initial begin
        clk = 1;
        reset = 1;

```

```

instruction = 10'b0000000000; // NOP
#8;
reset = 0;

instruction = 10'b1001000011; // addi $t1, $zero, 3
#8;
instruction = 10'b1000100010; // addi $t0, $zero, 2
#8;
instruction = 10'b1010110010; // sw $t0, 2($t1)
#8;
instruction = 10'b1011001111; // sw $t1, -1($t0)
#8;
instruction = 10'b1100110010; // lw $t0, 2($t1)
#8;
instruction = 10'b1101001111; // lw $t1, -1($t0)
#8;
instruction = 10'b1110000011; // halt
#8;
reset = 1;
end
endmodule

module CPU10Bits_shift_test();
    reg clk;
    reg reset;
    reg [9:0] instruction;
    wire done;

    CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

    //toggle clock every 4ns
    always #4 clk = ~clk;

    initial begin
        clk = 1;
        reset = 1;
        instruction = 10'b0000000000; // NOP
        #8;
        reset = 0;

        instruction = 10'b1001000011; // addi $t1, $zero, 3
        #8;
        instruction = 10'b0001010010; // add $t1, $t1, $t1
        #8;
        instruction = 10'b0001010010; // add $t1, $t1, $t1
        #8;
        instruction = 10'b1000100011; // addi $t0, $zero, 3
        #8;
        instruction = 10'b1001100101; // addi $s0, $zero, -3
        #8;
        instruction = 10'b0011001010; // sll $t1, $t1, $t0
        #8;
        instruction = 10'b0011011010; // sll $t1, $t1, $s0
        #8;
        instruction = 10'b1110000011; // halt
        #8;
        reset = 1;
    end
endmodule

module CPU10Bits_add_addi_test();
    reg clk;
    reg reset;

```

```

    reg [9:0] instruction;
    wire done;

    CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

//toggle clock every 4ns
always #4 clk = ~clk;

initial begin
    clk = 1;
    reset = 1;
    instruction = 10'b0000000000; // NOP
    #8;
    reset = 0;

    instruction = 10'b1001000011; // addi $t1, $zero, 3
    #8;
    instruction = 10'b0001010010; // add $t1, $t1, $t1
    #8;
    instruction = 10'b1000100011; // addi $t0, $zero, 3
    #8;
    instruction = 10'b1000101010; // addi $t0, $t0, 2
    #8;
    instruction = 10'b0001110001; // add $s0, $t1, $t0
    #8;
    instruction = 10'b1000101110; // addi $t0, $t0, -2
    #8;
    instruction = 10'b1001000111; // addi $t1, $zero, -1
    #8;
    instruction = 10'b1001100101; // addi $s0, $zero, -3
    #8;
    instruction = 10'b0000111010; // add $t0, $s0, $t1
    #8;
    instruction = 10'b1110000011; // halt
    #8;
    reset = 1;
end
endmodule

// Program 3, f = (x * y) - 4
// x = 3 -> $t1, y = 4 -> $s0, f = 8 -> $v0
// TEST 1
module CPU10Bits_program_test1();
    reg clk;
    reg reset;
    reg [9:0] instruction;
    wire done;

    integer x = 3;
    integer index = 0;
    integer x_neg = 0;

    CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

//toggle clock every 4ns
always #4 clk = ~clk;

initial begin
    clk = 1;
    reset = 1;
    instruction = 10'b0000000000; // NOP

```



```

#8;
reset = 0;
instruction = 10'b1001000011; // addi $t1, $zero, 3; $t1 = x
#8;
instruction = 10'b0011000101; // sll $a0, $t1, $zero
#8;
instruction = 10'b1001100010; // addi $s0, $zero, 2; $s0 = y
#8;
instruction = 10'b1001111010; // addi $s0, $s0, 2;
#8;
instruction = 10'b0000111000; // add $t0, $s0, $zero
#8;

for ( index = 0; index < (x - 1); index = index + 1 ) begin
    instruction = 10'b0111000000; //beq $t1, $zero, 0
    #8;
    instruction = 10'b0001111001; //add $s0, $s0, $t0
    #8;
    instruction = 10'b1001010111; //addi $t1, $t1, -1
    #8;
    instruction = 10'b1111110101; //j 11101 (-3)
    #8;
end
instruction = 10'b0001000101; // add $t1, $zero, $a0 ;load original x
#8;
instruction = 10'b0101000010; // cmp $t1, $t1, $zero
#8;
instruction = 10'b1000100001; // addi $t0, $zero, 1
#8;
instruction = 10'b0110110101; // beq $t0, $t1, -2 ;if x is pos,
pc=pc+2
#8;
if ( x_neg == 1 ) begin
    instruction = 10'b1001111100; // tcp $s0, $s0 ;two comp of
y
    #8;
end
instruction = 10'b1001111110; // addi $s0, $s0, -2;
#8;
instruction = 10'b1001111110; // addi $s0, $s0, -2;
#8;
instruction = 10'b0011100110; // sll $v0, $s0, $zero
#8;
instruction = 10'b1110000011; // halt
#8;
reset = 1;

end
endmodule

// Program 3, f = (x * y) - 4
// x = -5 -> $t1, y = 6 -> $s0, f = -34 -> $v0
// TEST 2
module CPU10Bits_program_test2();
    reg clk;
    reg reset;
    reg [9:0] instruction;
    wire done;

    integer x = 5;
    integer index = 0;
    integer x_neg = 1;

```

```

CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

//toggle clock every 4ns
always #4 clk = ~clk;

initial begin
    clk = 1;
    reset = 1;
    instruction = 10'b000000000; // NOP
    #8;
    reset = 0;
    instruction = 10'b1001000101; // addi $t1, $zero, -3; $t1 = x
    #8;
    instruction = 10'b1001010110; // addi $t1, $t1, -2; $t1 = x = -5
    #8;
    instruction = 10'b1001100011; // addi $s0, $zero, 3; $s0 = y =6
    #8;
    instruction = 10'b1001111011; // addi $s0, $s0, 3;
    #8;
    instruction = 10'b0000111000; // add $t0, $s0, $zero
    #8;

    for ( index = 0; index < (x - 1); index = index + 1 ) begin
        instruction = 10'b0111000000; //beq $t1, $zer0, 0
        #8;
        instruction = 10'b0001111001; //add $s0, $s0, $t0
        #8;
        instruction = 10'b1001010111; //addi $t1, $t1, -1
        #8;
        instruction = 10'b1111110101; //j 11101 (-3)
        #8;
    end
    instruction = 10'b0001000101; // add $t1, $zero, $a0 ;load original x
    #8;
    instruction = 10'b0101000010; // cmp $t1, $t1, $zer0
    #8;
    instruction = 10'b1000100001; // addi $t0, $zero, 1
    #8;
    instruction = 10'b0110110101; // beq $t0, $t1, -2 ;if x is pos,
pc=pc+2
    #8;
    if ( x_neg == 1 ) begin
        instruction = 10'b1001111100; // tcp $s0, $s0 ;two comp of
y
        #8;
    end
    instruction = 10'b1001111110; // addi $s0, $s0, -2;
    #8;
    instruction = 10'b1001111110; // addi $s0, $s0, -2;
    #8;
    instruction = 10'b0011100110; // sll $v0, $s0, $zer0
    #8;
    instruction = 10'b1110000011; // halt
    #8;
    reset = 1;

end

endmodule

// Program 3, f = (x * y) - 4
// x = 2 -> $t1, y = -8 -> $s0, f = -20 -> $v0

```

```

// TEST 3
module CPU10Bits_program_test3();
    reg clk;
    reg reset;
    reg [9:0] instruction;
    wire done;

    integer x = 2;
    integer index = 0;
    integer x_neg = 0;

    CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

//toggle clock every 4ns
always #4 clk = ~clk;

initial begin
    clk = 1;
    reset = 1;
    instruction = 10'b0000000000; // NOP
    #8;
    reset = 0;
    instruction = 10'b1001000010; // addi $t1, $zero, 2; $t1 = x
    #8;
    instruction = 10'b1001100101; // addi $s0, $zero, -3; $s0 = y
    #8;
    instruction = 10'b1001111101; // addi $s0, $s0, -3;
    #8;
    instruction = 10'b1001111110; // addi $s0, $s0, -2;
    #8;
    instruction = 10'b0000111000; // add $t0, $s0, $zero
    #8;

    for ( index = 0; index < (x - 1); index = index + 1 ) begin
        instruction = 10'b0111000000; //beq $t1, $zer0, 0
        #8;
        instruction = 10'b0001111001; //add $s0, $s0, $t0
        #8;
        instruction = 10'b1001010111; //addi $t1, $t1, -1
        #8;
        instruction = 10'b1111110101; //j 11101 (-3)
        #8;
    end
    instruction = 10'b0001000101; // add $t1, $zero, $a0 ;load original x
    #8;
    instruction = 10'b0101000010; // cmp $t1, $t1, $zer0
    #8;
    instruction = 10'b1000100001; // addi $t0, $zero, 1
    #8;
    instruction = 10'b0110110101; // beq $t0, $t1, -2 ;if x is pos,
pc=pc+2
    #8;
    if ( x_neg == 1 ) begin
        instruction = 10'b1001111100; // tcp $s0, $s0 ;two comp of
y
        #8;
    end
    instruction = 10'b1001111110; // addi $s0, $s0, -2;
    #8;
    instruction = 10'b1001111110; // addi $s0, $s0, -2;
    #8;
    instruction = 10'b0011100110; // sll $v0, $s0, $zer0
    #8;

```

```

        instruction = 10'b1110000011; // halt
        #8;
        reset = 1;

    end
endmodule

// Program 3, f = (x * y) - 4
// x = -5 -> $t1, y = -2 -> $s0, f = 6 -> $v0
// TEST 4
module CPU10Bits_program_test4();
    reg clk;
    reg reset;
    reg [9:0] instruction;
    wire done;

    integer x = 5;
    integer index = 0;
    integer x_neg = 1;

    CPU10Bits cpu0( .instruction(instruction), .clk(clk), .reset(reset), .done(done)
);

    //toggle clock every 4ns
    always #4 clk = ~clk;

    initial begin
        clk = 1;
        reset = 1;
        instruction = 10'b0000000000; // NOP
        #8;
        reset = 0;
        instruction = 10'b1001000101; // addi $t1, $zero, -3; $t1 = x
        #8;
        instruction = 10'b1001010110; // addi $t1, $t1, -2; $t1 = x=-5
        #8;
        instruction = 10'b1001100110; // addi $s0, $zero, -2; $s0 = y
        #8;
        instruction = 10'b0000111000; // add $t0, $s0, $zero
        #8;

        for ( index = 0; index < (x - 1); index = index + 1 ) begin
            instruction = 10'b0111000000; //beq $t1, $zero, 0
            #8;
            instruction = 10'b0001111001; //add $s0, $s0, $t0
            #8;
            instruction = 10'b1001010111; //addi $t1, $t1, -1
            #8;
            instruction = 10'b1111110101; //j 11101 (-3)
            #8;

        end
        instruction = 10'b0001000101; // add $t1, $zero, $a0 ;load original x
        #8;
        instruction = 10'b0101000010; // cmp $t1, $t1, $zero
        #8;
        instruction = 10'b1000100001; // addi $t0, $zero, 1
        #8;
        instruction = 10'b0110110101; // beq $t0, $t1, -2 ;if x is pos,
pc=pc+2
        #8;
        if ( x_neg == 1 ) begin
            instruction = 10'b1001111100; // tcp $s0, $s0 ;two comp of
y

```

```

        #8;
    end
    instruction = 10'b1001111110; // addi $s0, $s0, -2;
    #8;
    instruction = 10'b1001111110; // addi $s0, $s0, -2;
    #8;
    instruction = 10'b0011100110; // sll $v0, $s0, $zer0
    #8;
    instruction = 10'b1110000011; // halt
    #8;
    reset = 1;

end
endmodule

module CPU10Bits(
    input wire [9:0] instruction,
    input wire clk,
    input wire reset,
    output reg done
);

    wire [1:0] ALU_op;
    wire reg_write;
    wire [2:0] reg_write_addr; // destination select
    wire [9:0] alu_source1; // ALU input a
    wire [9:0] alu_source2; // ALU input b
    wire alu_source1_control;
    wire [1:0] alu_source2_control;
    wire [1:0] pc_control;
    wire [9:0] PC;
    wire c_out;
    wire [9:0] result;
    wire [2:0] reg_read1_addr; // source select
    wire [9:0] read1_data;
    wire [9:0] read2_data;

    ControlUnit cu0( .instruction(instruction), .ALU_op(ALU_op), .reg_write
(reg_write), .reg_write_addr(reg_write_addr), .reg_read1_addr
(reg_read1_addr), .alu_source1_control(alu_source1_control), .alu_source2_control
(alu_source2_control), .pc_control(pc_control) );

    FetchUnit fu0( .clk(clk), .reset(reset), .pc_control(pc_control), .branch_control
(result), .jump_address(instruction[6:2]), .branch_address(instruction
[2:0]), .reg_address(read1_data), .PC_out(PC) );

    RegisterFile rf( .clk(clk), .reset(reset), .en_write(reg_write), .write_addr
(reg_write_addr), .write_data(result), .read1_addr(reg_read1_addr), .read2_addr
(instruction[4:3]), .read1_data(read1_data), .read2_data(read2_data) );

    ALU alu0( .ALU_op(ALU_op), .a(alu_source1), .b(alu_source2), .f(result), .c_out
(c_out) );

    ALU_source1_mux asm1( .alu_source1_select(alu_source1_control), .reg_read1_data
(read1_data), .pc(PC), .alu_source(alu_source1) );

    ALU_source2_mux asm2( .alu_source2_select(alu_source2_control), .reg_read2_data
(read2_data), .imm(instruction[2:0]), .jump_link_offset(10'b0000000001), .alu_source
(alu_source2) );

    always@(*) begin
        // halt
        if ( instruction[9:7] == 3'b111 && instruction[1:0] == 2'b11 ) begin

```

```

        done <= 1'b1;
    end
    else begin
        done <= 1'b0;
    end
end

endmodule

// ALU Source 1 Mux
// alu_source1_select:
// 0 -> reg_read1_data
// 1 -> PC
module ALU_source1_mux(
    input wire alu_source1_select,
    input wire [9:0]reg_read1_data,
    input wire [9:0]pc,
    output reg [9:0]alu_source
);
    always@(*)begin
        case(alu_source1_select)
            1'b1: alu_source <= pc;
            1'b0: alu_source <= reg_read1_data;
            default: alu_source <= reg_read1_data;
        endcase
    end
endmodule

// ALU Source 2 Mux
// alu_source2_select:
// 00 -> reg_read2_data
// 01 -> imm - sign extend
// 10 -> jump_link_offset
module ALU_source2_mux(
    input wire [1:0]alu_source2_select,
    input wire [9:0]reg_read2_data,
    input wire [2:0]imm,
    input wire [9:0]jump_link_offset,
    output reg [9:0]alu_source
);
    always@(*)begin
        case(alu_source2_select)
            2'b00: alu_source <= reg_read2_data;
            2'b01: alu_source <= { {7{imm[2]}}, imm[2:0] }; //sign extend imm
            2'b10: alu_source <= jump_link_offset;
            default: alu_source <= reg_read2_data;
        endcase
    end
endmodule

```

```

`timescale 1ns / 1ns
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company: Western Michigan University
// Engineer: Tyler Thompson
//
// Create Date: 02/22/2018 03:55:32 PM
// Design Name:
// Module Name: ControlUnit
// Project Name: ECE 3570 Lab 3a
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

```

```

module ControlUnitTest();
    reg [9:0] instruction;
    wire [1:0] ALU_op;
    wire reg_write;
    wire [2:0] reg_write_addr;
    wire [2:0] reg_read1_addr;
    wire alu_source1_control;
    wire [1:0] alu_source2_control;
    wire [1:0] pc_control;

    ControlUnit cu0( .instruction(instruction), .ALU_op(ALU_op), .reg_write
(reg_write), .reg_write_addr(reg_write_addr), .reg_read1_addr
(reg_read1_addr), .alu_source1_control(alu_source1_control), .alu_source2_control
(alu_source2_control), .pc_control(pc_control) );

```

```

initial begin
    instruction = 10'b0000000000;
    #8;

    instruction = 10'b1001000011; // addi $t1, $zero, 3
    #8;
    instruction = 10'b1001010011; // addi $t1, $t1, 3
    #8;
    instruction = 10'b1001010011; // addi $t1, $t1, 3
    #8;
    instruction = 10'b1000100001; // addi $t0, $zero, 1
    #8;
    instruction = 10'b1011001111; // sw $t1, -1($t0)
    #8;
    instruction = 10'b1100110010; // lw $t0, 2($t1)
    #8;
    instruction = 10'b0001101010; // add $s0, $t0, $t1
    #8;
    instruction = 10'b0001111010; // add $s0, $s0, $t1
    #8;
    instruction = 10'b1001111100; // tpc $s0, $s0
    #8;
    instruction = 10'b0011110001; // sll $t0, $s0, $t1
    #8;
    instruction = 10'b0110100011; // beq $t0, $zero, PC=PC+4+3
    #8;
    instruction = 10'b1001010011; // addi $t1, $t1, 3
    #8;

```

```

instruction = 10'b0110110011; // beq $t0, $t1, PC=PC+4+3
#8;
instruction = 10'b1110001100; // jr $s0
#8;
instruction = 10'b1110111101; // j 01111 (15)
#8;
instruction = 10'b1111000010; // jal 10000 (-16)
#8;
instruction = 10'b1001010011; // addi $t1, $t1, 3
#8;
instruction = 10'b1110011100; // jr $ra
#8;
instruction = 10'b1001010011; // addi $t1, $t1, 3
#8;
instruction = 10'b0101110001; // cmp $t0, $s0, $t1
#8;
instruction = 10'b1110000011; // halt
#8;

```

**end**

**endmodule**

```

module ControlUnit(
    input wire [9:0] instruction,
    output reg [1:0] ALU_op,
    output reg reg_write,
    output reg [2:0] reg_write_addr,
    output reg [2:0] reg_read1_addr,
    output reg alu_source1_control,
    output reg [1:0] alu_source2_control,
    output reg [1:0] pc_control
);

    reg [2:0] op_code;
    reg [1:0] funct_code;
    reg [1:0] rs_addr;
    reg [1:0] rt_addr;
    reg [2:0] rd_addr; //also hold immediate value for I type instructions
    reg [4:0] j_addr;

    wire reg_write_mux_val;
    reg_write_mux rwm0( .op_code(op_code), .funct_code(funct_code), .reg_write
(reg_write_mux_val) );

    wire [1:0] ALU_op_mux_val;
    ALU_op_mux aom0( .op_code(op_code), .rd_addr(rd_addr), .tcp(2'b11), .ALU_op
(ALU_op_mux_val) );

    wire [1:0] pc_control_mux_val;
    pc_control_mux pcm0( .op_code(op_code), .funct_code(funct_code), .pc_control
(pc_control_mux_val) );

    wire [2:0] reg_write_addr_control_val;
    reg_write_addr_control_mux rwacm0( .op_code(op_code), .rd_addr(rd_addr), .rs_addr
(rs_addr), .write_addr(reg_write_addr_control_val) );

    wire [2:0] reg_read1_addr_mux_val;
    reg_read1_addr_mux rram0( .op_code(op_code), .funct_code(funct_code), .rd_addr
(rd_addr), .rs_addr(rs_addr), .rt_addr(rt_addr), .j_addr(j_addr), .read_addr
(reg_read1_addr_mux_val) );

```



```

    wire alu_source1_control_mux_val;
    ALU_source1_control_mux asm1( .op_code(op_code), .funct_code(funct_code), .control
(alu_source1_control_mux_val) );

    wire [1:0] alu_source2_control_mux_val;
    ALU_source2_control_mux asm2( .op_code(op_code), .funct_code(funct_code), .control
(alu_source2_control_mux_val) );

    always@(*) begin
        // instruction decode
        op_code <= instruction[9:7];
        funct_code <= instruction[1:0];
        rs_addr <= instruction[6:5];
        rt_addr <= instruction[4:3];
        rd_addr <= instruction[2:0];
        j_addr <= instruction[6:2];

        reg_write <= reg_write_mux_val;
        ALU_op <= ALU_op_mux_val;
        pc_control <= pc_control_mux_val;
        reg_write_addr <= reg_write_addr_control_val;
        reg_read1_addr <= reg_read1_addr_mux_val;
        alu_source1_control <= alu_source1_control_mux_val;
        alu_source2_control <= alu_source2_control_mux_val;

    end

endmodule

// read1_addr
module reg_read1_addr_mux(
    input wire [2:0] op_code,
    input wire [1:0] funct_code,
    input wire [2:0] rd_addr,
    input wire [1:0] rs_addr,
    input wire [1:0] rt_addr,
    input wire [4:0] j_addr,
    output reg [2:0] read_addr
);
    always@(*)begin
        case(op_code)
            3'b000: read_addr <= rd_addr; // add
            3'b100: read_addr <= rt_addr; // addi
            3'b101: read_addr <= rt_addr; // sw
            3'b110: read_addr <= rt_addr; // lw
            3'b111: begin
                case(funct_code)
                    2'b00: read_addr <= j_addr; // jr
                    default: read_addr <= rs_addr;
                endcase
            end
            default: read_addr <= rs_addr;
        endcase
    end
endmodule

module reg_write_addr_control_mux(
    input wire [2:0] op_code,
    input wire [2:0] rd_addr,
    input wire [1:0] rs_addr,
    output reg [2:0] write_addr
);
    always@(*)begin

```

```

        case(op_code)
            3'b000: write_addr <= rs_addr; // add
            3'b100: write_addr <= rs_addr; // addi
            3'b110: write_addr <= rs_addr; // lw
            3'b101: write_addr <= rs_addr; // sw
            3'b111: write_addr <= 3'b111; // jal
            default: write_addr <= rd_addr;
        endcase
    end
endmodule

// ALU Source 1 Control
// control:
// 0 -> reg_read1_data
// 1 -> PC
module ALU_source1_control_mux(
    input wire [2:0] op_code,
    input wire [1:0] funct_code,
    output reg control
);
    always@(*) begin
        case(op_code)
            3'b111: begin
                case(funct_code)
                    2'b10: control <= 1'b1; // jal
                    default: control <= 1'b0;
                endcase
            end
            default: control <= 0;
        endcase
    end
endmodule

// ALU Source 2 Control
// control:
// 00 -> reg_read2_data
// 01 -> imm - sign extend
// 10 -> jump_link_offset
module ALU_source2_control_mux(
    input wire [2:0] op_code,
    input wire [1:0] funct_code,
    output reg [1:0] control
);
    always@(*) begin
        case(op_code)
            3'b100: control <= 1'b01; // addi
            3'b110: control <= 1'b01; // lw
            3'b101: control <= 1'b01; // sw
            3'b111: begin
                case(funct_code)
                    2'b10: control <= 2'b10; // jal
                    default: control <= 1'b00;
                endcase
            end
            default: control <= 1'b00;
        endcase
    end
endmodule

module pc_control_mux(
    input wire [2:0] op_code,
    input wire [1:0] funct_code,
    output reg [1:0] pc_control
);

```

```

always@(*) begin
    case(op_code)
        3'b011: pc_control <= 2'b11; // beq - branch
        3'b111: begin // J-type
            case(funcnt_code)
                2'b00: pc_control <= 2'b10; // jump_reg
                default: pc_control <= 2'b01; // jump
            endcase
        end
        default: pc_control <= 2'b00;
    endcase
end

endmodule

module ALU_op_mux(
    input wire [2:0] op_code,
    input wire [2:0] rd_addr,
    input wire [1:0] tcp,
    output reg [1:0] ALU_op
);

always@(*) begin
    case(op_code)
        //3'b000: ALU_op <= 2'b00; //add
        3'b001: ALU_op <= 2'b10; //sll
        3'b010: ALU_op <= 2'b01; //cmp
        3'b011: ALU_op <= 2'b01; //beq
        3'b100: begin
            case(rd_addr)
                3'b100: ALU_op <= tcp; //tcp Twos complement
                default: ALU_op <= 2'b00; //addi
            endcase
        end
        default: ALU_op <= 2'b00;
    endcase
end

endmodule

module reg_write_mux(
    input wire [2:0] op_code,
    input wire [1:0] funct_code,
    output reg reg_write
);
always@(*) begin
    case(op_code)
        3'b011: reg_write <= 0; //beq
        3'b101: reg_write <= 0; //sw:
        3'b111: begin // j-type
            case(funcnt_code)
                2'b10: reg_write <= 1; // jal
                default: reg_write <= 0;
            endcase
        end
        default: reg_write <= 1;
    endcase
end

endmodule

```

```

`timescale 1ns / 1ns
`include "ALU.v"
`include "Registers.v"

/////////////////////////////////////////////////////////////////
// Company: Western Michigan University
// Engineer: Tyler Thompson
//
// Create Date: 02/13/2018 02:47:56 PM
// Design Name:
// Module Name: FetchUnit
// Project Name: ECE 3570 Lab 2
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies: ALU.v, Registers.v
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
/////////////////////////////////////////////////////////////////

module FetchUnitTest();
    reg clk, reset;
    reg [1:0] pc_control;
    reg [9:0] branch_control;
    reg [4:0] jump_address;
    reg [2:0] branch_address;
    reg [9:0] reg_address;
    wire [9:0] PC;
    //toggle clock every 5ns
    always #5 clk = ~clk;

    FetchUnit fu0( .clk(clk), .reset(reset), .pc_control(pc_control), .branch_control
(branch_control), .jump_address(jump_address), .branch_address
(branch_address), .reg_address(reg_address), .PC_out(PC) );

    initial begin
        branch_control = 1;
        clk = 0;
        reset = 1; //initialize the program counter
        #20
        reset = 0;
        #15

        pc_control = 2'b00; // increment program counter by 1
        #20
        pc_control = 2'b01; jump_address = 5'b00100; // increment program count by 4
        #20
        pc_control = 2'b10; reg_address = 10'b0001000000; // set program counter to 64
        #20
        pc_control = 2'b11; branch_address = 3'b010; branch_control = 0; // branch to
address
        #20
        pc_control = 2'b00;
    end
endmodule

// Program Counter control unit

```

```

// pc_control: 00 -> increment program count by 1
//             01 -> add jump_address to program counter
//             10 -> set program counter to reg_address
//             11 -> add 4 to program count and then add the branch_address
module FetchUnit(
    input wire clk,
    input wire reset,
    input wire [1:0] pc_control,
    input wire [9:0] branch_control,
    input wire [4:0] jump_address,
    input wire [2:0] branch_address,
    input wire [9:0] reg_address,
    output wire [9:0] PC_out
);
    reg [9:0] PC_in;
    reg [9:0] b;
    wire c_out;
    wire [9:0] sum;
    wire [9:0] branch_offset;
    reg [9:0] branch_ext;

    //Create 10 bit register for program counter
    Register_10bit pc_reg( .clk(clk), .reset(reset), .Din(PC_in), .Dout(PC_out) );

    //adder for calculating branch offset
    FullAdder_10Bit fal( .a( branch_ext ), .b(10'b0000000100), .sum
(branch_offset), .c_out(c_out) );

    //adder for calculating pc address
    FullAdder_10Bit fa0( .a(PC_out), .b(b), .sum(sum), .c_out(c_out) );

    //update the program counter on each clock cycle
    always @(*) begin
        //sign extend branch address
        branch_ext <= { {7{branch_address[2]}}, branch_address[2:0] };
        PC_in <= sum;
        b <= 0;
        if ( reset == 0 ) begin
            case(pc_control)
                2'b00: b <= 10'b0000000001;
                2'b01: b <= { {5{jump_address[4]}}, jump_address[4:0] }; // sign
            extend jump address
                2'b10: PC_in <= reg_address;
                2'b11: begin // branch
                    if ( branch_control == 0 ) begin
                        b <= branch_offset;
                    end
                    else begin
                        b <= 10'b0000000001;
                    end
                end
                default: PC_in <= PC_out;
            endcase
        end
        else begin
            PC_in <= 0;
        end
    end

end

endmodule

```

```

`timescale 1ns / 1ns
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company: Western Michigan University
// Engineer: Tyler Thompson
//
// Create Date: 02/13/2018 02:44:18 PM
// Design Name:
// Module Name: ALU
// Project Name: ECE 3570 Lab 2
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

module ALUTest();

    wire [9:0] result;
    wire c_out;

    reg [9:0] a;
    reg [9:0] b;
    reg [1:0] ALU_op;

    ALU alu0( .ALU_op(ALU_op), .a(a), .b(b), .f(result), .c_out(c_out) );

    initial begin
        ALU_op = 2'b00;
        a = 10'b0000000000;
        b = 10'b0000000000;
    end

    always @(a or b) begin
        //adder test
        a = 10'b0000000001; b = 10'b0000000001; ALU_op = 2'b00; // 1 + 1
        #8;
        a = 10'b0000000011; b = 10'b0000000001; ALU_op = 2'b00; // 3 + 1
        #8;
        a = 10'b0000000010; b = 10'b0000000001; ALU_op = 2'b00; // 2 + 1
        #8;
        a = 10'b0010110010; b = 10'b0011001101; ALU_op = 2'b00; // 178 + 205 = 383
        #8;
        a = 10'b1101001110; b = 10'b0011001101; ALU_op = 2'b00; // -178 + 205 = 27
        #8;
        a = 10'b1101001110; b = 10'b1111111110; ALU_op = 2'b00; // -178 + -2 = -180
        #8;

        //shifter test
        a = 10'b0001000000; b = 10'b1111111111; ALU_op = 2'b10; //shift a right by 1
        #8;
        a = 10'b0000000001; b = 10'b0000000001; ALU_op = 2'b10; //shift a left by 1
        #8;
        a = 10'b0001000000; b = 10'b1111111100; ALU_op = 2'b10; //shift a right by 4
        #8;
        a = 10'b0000000001; b = 10'b0000000100; ALU_op = 2'b10; //shift a left by 4
        #8;
    end
endmodule

```

```

        //comparator test
        a = 10'b0000000010; b = 10'b0000000001; ALU_op = 2'b01; //test if 2 is
greater than 1
        #8;
        a = 10'b0000000001; b = 10'b0000000010; ALU_op = 2'b01; //test if 1 is
greater than 2
        #8;
        a = 10'b0000000001; b = 10'b0000000001; ALU_op = 2'b01; //test if 1 is
greater than 1
        #8;
        a = 10'b1111111111; b = 10'b0000000001; ALU_op = 2'b01; //test if -1 is
greater than 1
        #8;
        a = 10'b0000000001; b = 10'b1111111111; ALU_op = 2'b01; //test if 1 is
greater than -1
        #8;
        a = 10'b1111111110; b = 10'b1111111111; ALU_op = 2'b01; //test if -2 is
greater than -1
        #8;
        a = 10'b1111111111; b = 10'b1111111110; ALU_op = 2'b01; //test if -1 is
greater than -2
        #8;
        a = 10'b1111110000; b = 10'b1111111100; ALU_op = 2'b01; //test if -16 is
greater than -4
        #8;
        a = 10'b1111111000; b = 10'b1111101100; ALU_op = 2'b01; //test if -8 is
greater than -20
        #8;
        a = 10'b1000000000; b = 10'b1000000010; ALU_op = 2'b01; //test if -512 is
greater than -510
        #8;
        a = 10'b1000000010; b = 10'b1000000000; ALU_op = 2'b01; //test if -510 is
greater than -512
        #8;
        a = 10'b0111111111; b = 10'b0111111110; ALU_op = 2'b01; //test if 511 is
greater than 510
        end
endmodule

```

**endmodule**

```

// Arithmetic Logic Unit
// Supports add, shift, and compare operations
// ALU_op: 00 -> adder
//          01 -> comparator
//          10 -> shifter
//          11 -> Twos Complement
module ALU(
    input wire [1:0] ALU_op,
    input wire [9:0] a,
    input wire [9:0] b,
    output wire [9:0] f,
    output c_out
);
    wire [9:0] add_result;
    wire [9:0] shift_result;
    wire [9:0] comp_result;
    wire [9:0] complement_result;

    FullAdder_10Bit fa0( .a(a), .b(b), .sum(add_result), .c_out(c_out) );
    Comparator cp0( .a(a), .b(b), .out(comp_result) );
    Shifter sh0( .a(a), .shift_amount(b), .out(shift_result) );
    Complementor cptr0( .a(a), .out(complement_result) );
    ALU_mux mx0( .ALU_op(ALU_op), .add_result(add_result), .comp_result

```



```
(comp_result), .shift_result(shift_result), .complement_result
(complement_result), .final_answer(f) );
```

```
endmodule
```

```
// Multiplexer for ALU output selection
```

```
// ALU_op: 00 -> adder
```

```
//          01 -> comparator
```

```
//          10 -> shifter
```

```
//          11 -> complementor
```

```
module ALU_mux(
```

```
    input wire [1:0] ALU_op,
```

```
    input wire [9:0] add_result,
```

```
    input wire [9:0] comp_result,
```

```
    input wire [9:0] shift_result,
```

```
    input wire [9:0] complement_result,
```

```
    output reg [9:0] final_answer
```

```
);
```

```
    always@(*) begin
```

```
        case(ALU_op)
```

```
            2'b00: final_answer <= add_result;
```

```
            2'b01: final_answer <= comp_result;
```

```
            2'b10: final_answer <= shift_result;
```

```
            2'b11: final_answer <= complement_result;
```

```
            default: final_answer <= 10'b0;
```

```
        endcase
```

```
    end
```

```
endmodule
```

```
// takes the twos complement of an input.
```

```
module Complementor(
```

```
    input wire [9:0] a,
```

```
    output reg [9:0] out
```

```
);
```

```
    reg [9:0] not_a;
```

```
    wire c_out;
```

```
    wire [9:0] sum;
```

```
    FullAdder_10Bit fa1( .a(not_a), .b(10'b000000001), .sum(sum), .c_out(c_out) );
```

```
    always@(*)begin
```

```
        not_a <= ~a;
```

```
        out <= sum;
```

```
    end
```

```
endmodule
```

```
// Compares a to b
```

```
// out = 2 if a is greater than b and 0 if a is equal to b and 1 if a is less than b
```

```
module Comparator(
```

```
    input wire [9:0] a,
```

```
    input wire [9:0] b,
```

```
    output reg [9:0] out //2 -> a is greater than b, 0 -> a equal to b, 1-> a is less than b
```

```
);
```

```
    reg [9:0]temp0;
```

```
    wire [9:0] temp1;
```

```
    wire c_out;
```

```
    wire [9:0]sum;
```

```
    wire c_out1;
```

```
    //adder for twos complement
```

```

FullAdder_10Bit fa1( .a(10'b0000000001), .b(temp0), .sum(temp1), .c_out(c_out) );

FullAdder_10Bit fa2( .a(b), .b(temp1), .sum(sum), .c_out(c_out1) );
always@(*) begin
    temp0 <= 0;
    // a and b are equal
    if ( a == b ) begin
        out = 10'b0000000000;
    end
    //both a and b are negative
    else if ( (a[9] & b[9]) == 1 ) begin
        //twos complement of a
        temp0 <= ~a;

        if (c_out1 == 1) begin
            out = 10'b0000000001;
        end
        else begin
            out = 10'b0000000010;
        end
    end
    //a is negative and b is positive
    else if ( a[9] == 1 ) begin
        out = 10'b0000000001;
    end
    //a is positive and b is negative
    else if ( b[9] == 1 ) begin
        out = 10'b0000000010;
    end
    //a is positive and b is positive
    else begin
        //twos complement of a
        temp0 <= ~a;

        if ( sum[9] == 1 ) begin
            out = 10'b0000000010;
        end
        else begin
            out = 10'b0000000001;
        end
    end
end

end
endmodule

```

```

// Shift a number left or right
// a positive shift_amount value will shift the number left
// a negative shift_amount value will shift the number right
module Shifter(
    input [9:0] a,
    input [9:0] shift_amount,
    output reg [9:0] out
);
    reg [9:0] x;
    wire [9:0] sum;
    wire c_out;
    FullAdder_10Bit fa2( .a(x), .b(10'b0000000001), .sum(sum), .c_out(c_out) );
    always @(*) begin
        //if shift_amount is negative, take twos complement and shift right
        if ( shift_amount[9] == 1'b1 ) begin
            x <= ~shift_amount ;
        end
    end
endmodule

```

```

        out = a >> sum;
    end
    else begin
        out = a << shift_amount;
        x <= 0;
    end
end
endmodule

// Ripple adder for 10 bit numbers
module FullAdder_10Bit(
    input [9:0] a,
    input [9:0] b,
    output [9:0] sum,
    output c_out
);
    wire [8:0] ripple;

    FullAdder_1Bit f0( .a( a[0] ), .b( b[0] ), .c_in( 1'b0 ), .s( sum[0] ), .c_out
( ripple[0] ) );
    FullAdder_1Bit f1( .a( a[1] ), .b( b[1] ), .c_in( ripple[0] ), .s( sum
[1] ), .c_out( ripple[1] ) );
    FullAdder_1Bit f2( .a( a[2] ), .b( b[2] ), .c_in( ripple[1] ), .s( sum
[2] ), .c_out( ripple[2] ) );
    FullAdder_1Bit f3( .a( a[3] ), .b( b[3] ), .c_in( ripple[2] ), .s( sum
[3] ), .c_out( ripple[3] ) );
    FullAdder_1Bit f4( .a( a[4] ), .b( b[4] ), .c_in( ripple[3] ), .s( sum
[4] ), .c_out( ripple[4] ) );
    FullAdder_1Bit f5( .a( a[5] ), .b( b[5] ), .c_in( ripple[4] ), .s( sum
[5] ), .c_out( ripple[5] ) );
    FullAdder_1Bit f6( .a( a[6] ), .b( b[6] ), .c_in( ripple[5] ), .s( sum
[6] ), .c_out( ripple[6] ) );
    FullAdder_1Bit f7( .a( a[7] ), .b( b[7] ), .c_in( ripple[6] ), .s( sum
[7] ), .c_out( ripple[7] ) );
    FullAdder_1Bit f8( .a( a[8] ), .b( b[8] ), .c_in( ripple[7] ), .s( sum
[8] ), .c_out( ripple[8] ) );
    FullAdder_1Bit f9( .a( a[9] ), .b( b[9] ), .c_in( ripple[8] ), .s( sum
[9] ), .c_out( c_out ) );

endmodule

//simple adder for adding two bits
module FullAdder_1Bit(
    input wire a,
    input wire b,
    input wire c_in, //carry in
    output wire s, //sum
    output wire c_out //carry out
);

    assign s = a ^ b ^ c_in;
    assign c_out = ((a ^ b) & c_in) | (a & b);

endmodule

```

```

`timescale 1ns / 1ns
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////
// Company: Western Michigan University
// Engineer: Tyler Thompson
//
// Create Date: 02/05/2018 07:30:26 PM
// Design Name:
// Module Name: Registers
// Project Name: ECE 3570 Lab 2
// Target Devices:
// Tool Versions:
// Description:
//
// Dependencies:
//
// Revision:
// Revision 0.01 - File Created
// Additional Comments:
//
////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////////

module RegisterFileTest();
    reg clk;
    reg en_write;
    reg [2:0] write_addr;
    reg [9:0] write_data;
    reg [2:0] read1_addr;
    reg [2:0] read2_addr;
    wire [9:0] read1_data;
    wire [9:0] read2_data;

    //toggle clock every 4ns
    always #4 clk = ~clk;

    RegisterFile rf( .clk(clk), .en_write(en_write), .write_addr
(write_addr), .write_data(write_data), .read1_addr(read1_addr), .read2_addr
(read2_addr), .read1_data(read1_data), .read2_data(read2_data) );

    initial begin
        en_write = 0;
        clk = 0;
        #4;
        //prove you can't write to the zero register
        en_write = 1; write_addr = 3'b000; write_data = 10'b1111111111; read1_addr =
3'b000; read2_addr = 3'b000;
        #8;
        //write to $t0 and read $zero twice
        en_write = 1; write_addr = 3'b001; write_data = 10'b0000001111; read1_addr =
3'b000; read2_addr = 3'b000;
        #8;
        //write to $t1 and read $t0 and $zero
        en_write = 1; write_addr = 3'b010; write_data = 10'b1010101010; read1_addr =
3'b001; read2_addr = 3'b000;
        #8;
        //write to $s0 and read $t1 and $t0
        en_write = 1; write_addr = 3'b011; write_data = 10'b0101010101; read1_addr =
3'b010; read2_addr = 3'b001;
        #8;
        //write to $sp and read $s0 and $t1
        en_write = 1; write_addr = 3'b100; write_data = 10'b1111000000; read1_addr =
3'b011; read2_addr = 3'b010;
        #8;
        //write to $a0 and read $sp and $s0
        en_write = 1; write_addr = 3'b101; write_data = 10'b0000111111; read1_addr =

```

```

3'b100; read2_addr = 3'b011;
#8;
//write to $v0 and read $a0 and $sp
en_write = 1; write_addr = 3'b110; write_data = 10'b1111111111; read1_addr =
3'b101; read2_addr = 3'b100;
#8;
//write to $ra and read $v0 and $a0
en_write = 1; write_addr = 3'b111; write_data = 10'b1100110011; read1_addr =
3'b110; read2_addr = 3'b101;
#8;
//read from $ra and $v0
en_write = 0; read1_addr = 3'b111; read2_addr = 3'b110;

    end
endmodule

```

```

// Register file, read and write data to registers
// addressing: 000 -> $zero
//              001 -> $t0
//              010 -> $t1
//              011 -> $s0
//              100 -> $sp
//              101 -> $a0
//              110 -> $v0
//              111 -> $ra
module RegisterFile(
    input wire clk,
    input wire reset,
    input wire en_write,
    input wire [2:0] write_addr,
    input wire [9:0] write_data,
    input wire [2:0] read1_addr,
    input wire [1:0] read2_addr,
    output reg [9:0] read1_data,
    output reg [9:0] read2_data
);

    //Array of data input for registers
    reg [9:0]Din [7:0];

    //Array of data outputs for registers
    wire [9:0]Dout[7:0];

    //reg [2:0] read1_addr_ext;
    //wire reset = 0;
    //Initialize all general purpose registers
    Register_10bit reg_zero(.clk(clk), .reset(1'b1), .Din(Din[0]), .Dout(Dout[0]));
    Register_10bit reg_t0(.clk(clk), .reset(reset), .Din(Din[1]), .Dout(Dout[1]));
    Register_10bit reg_t1(.clk(clk), .reset(reset), .Din(Din[2]), .Dout(Dout[2]));
    Register_10bit reg_s0(.clk(clk), .reset(reset), .Din(Din[3]), .Dout(Dout[3]));
    Register_10bit reg_sp(.clk(clk), .reset(reset), .Din(Din[4]), .Dout(Dout[4]));
    Register_10bit reg_a0(.clk(clk), .reset(reset), .Din(Din[5]), .Dout(Dout[5]));
    Register_10bit reg_v0(.clk(clk), .reset(reset), .Din(Din[6]), .Dout(Dout[6]));
    Register_10bit reg_ra(.clk(clk), .reset(reset), .Din(Din[7]), .Dout(Dout[7]));

    always@(*) begin
        Din[0] <= Dout[0]; Din[1] <= Dout[1]; Din[2] <= Dout[2]; Din[3] <= Dout[3];
        Din[4] <= Dout[4]; Din[5] <= Dout[5]; Din[6] <= Dout[6]; Din[7] <= Dout[7];
        read1_data <= Dout[read1_addr];
        read2_data <= Dout[read2_addr];
        if ( en_write == 1 ) begin
            Din[write_addr] <= write_data;
        end
    end

```

```

        end

endmodule

module RegisterTest();
    reg clk, reset;
    //toggle clock every 4ns
    always #4 clk = ~clk;

    //Array of data input for registers
    reg [9:0]Din [7:0];

    //Array of data outputs for registers
    wire [9:0]Dout[7:0];

    //Initialize all general purpose registers
    Register_10bit reg_zero(.clk(clk), .reset(1'b1), .Din(Din[0]), .Dout(Dout[0]));
    Register_10bit reg_t0(.clk(clk), .reset(reset), .Din(Din[1]), .Dout(Dout[1]));
    Register_10bit reg_t1(.clk(clk), .reset(reset), .Din(Din[2]), .Dout(Dout[2]));
    Register_10bit reg_s0(.clk(clk), .reset(reset), .Din(Din[3]), .Dout(Dout[3]));
    Register_10bit reg_sp(.clk(clk), .reset(reset), .Din(Din[4]), .Dout(Dout[4]));
    Register_10bit reg_a0(.clk(clk), .reset(reset), .Din(Din[5]), .Dout(Dout[5]));
    Register_10bit reg_v0(.clk(clk), .reset(reset), .Din(Din[6]), .Dout(Dout[6]));
    Register_10bit reg_ra(.clk(clk), .reset(reset), .Din(Din[7]), .Dout(Dout[7]));

    //run a test on the registers
    integer i;
    always @(posedge clk) begin
        for( i = 0; i < 8; i = i + 1) begin
            Din[i] = ~Dout[i];
            #4;
        end
    end

    initial begin
        clk = 0;
        reset = 0;

        //initialize all registers with zeros
        { Din[0], Din[1], Din[2], Din[3], Din[4], Din[5], Din[6], Din[7] } = { 10'b0,
10'b0, 10'b0, 10'b0, 10'b0, 10'b0, 10'b0, 10'b0 };
    end

endmodule

module Register_10bit(
    input wire clk,
    input wire reset,
    input wire [9:0] Din,
    output reg [9:0] Dout
);

    always @(posedge clk) begin
        if (reset == 1'b1) begin
            Dout <= 10'b0000000000;
        end
        else begin
            Dout <= Din;
        end
    end

endmodule

```